

# CHAPTER 20

## CONTROL UNIT OPERATION

### **20.1 Micro-Operations**

- The Fetch Cycle
- The Indirect Cycle
- The Interrupt Cycle
- The Execute Cycle
- The Instruction Cycle

### **20.2 Control of the Processor**

- Functional Requirements
- Control Signals
- A Control Signals Example
- Internal Processor Organization
- The Intel 8085

### **20.3 Hardwired Implementation**

- Control Unit Inputs
- Control Unit Logic

### **20.4 Key Terms, Review Questions, and Problems**

**LEARNING OBJECTIVES**

After studying this chapter, you should be able to:

- ◆ Explain the concept of micro-operations and define the principal instruction cycle phases in terms of micro-operations.
- ◆ Discuss how micro-operations are organized to control a processor.
- ◆ Understand hardwired control unit organization.

In Chapter 12, we pointed out that a machine instruction set goes a long way toward defining the processor. If we know the machine instruction set, including an understanding of the effect of each opcode and an understanding of the addressing modes, and if we know the set of user-visible registers, then we know the functions that the processor must perform. This is not the complete picture. We must know the external interfaces, usually through a bus, and how interrupts are handled. With this line of reasoning, the following list of those things needed to specify the function of a processor emerges:

1. Operations (opcodes)
2. Addressing modes
3. Registers
4. I/O module interface
5. Memory module interface
6. Interrupts

This list, though general, is rather complete. Items 1 through 3 are defined by the instruction set. Items 4 and 5 are typically defined by specifying the system bus. Item 6 is defined partially by the system bus and partially by the type of support the processor offers to the operating system.

This list of six items might be termed the functional requirements for a processor. They determine what a processor must do. This is what occupied us in Parts Two and Four. Now, we turn to the question of how these functions are performed or, more specifically, how the various elements of the processor are controlled to provide these functions. Thus, we turn to a discussion of the control unit, which controls the operation of the processor.

## 20.1 MICRO-OPERATIONS

We have seen that the operation of a computer, in executing a program, consists of a sequence of instruction cycles, with one machine instruction per cycle. Of course, we must remember that this sequence of instruction cycles is not necessarily the same as the *written sequence* of instructions that make up the program, because of the existence of branching instructions. What we are referring to here is the *execution time sequence* of instructions.

We have further seen that each instruction cycle is made up of a number of smaller units. One subdivision that we found convenient is fetch, indirect, execute, and interrupt, with only fetch and execute cycles always occurring.


To design a control unit, however, we need to break down the description further. In our discussion of pipelining in Chapter 14, we began to see that a further decomposition is possible. In fact, we will see that each of the smaller cycles involves a series of steps, each of which involves the processor registers. We will refer to these steps as **micro-operations**. The prefix *micro* refers to the fact that each step is very simple and accomplishes very little. Figure 20.1 depicts the relationship among the various concepts we have been discussing. To summarize, the execution of a program consists of the sequential execution of instructions. Each instruction is executed during an instruction cycle made up of shorter subcycles (e.g., fetch, indirect, execute, interrupt). The execution of each subcycle involves one or more shorter operations, that is, micro-operations.

Micro-operations are the functional, or atomic, operations of a processor. In this section, we will examine micro-operations to gain an understanding of how the events of any instruction cycle can be described as a sequence of such micro-operations. A simple example will be used. In the remainder of this chapter, we then show how the concept of micro-operations serves as a guide to the design of the control unit.

## The Fetch Cycle

We begin by looking at the fetch cycle, which occurs at the beginning of each instruction cycle and causes an instruction to be fetched from memory. For purposes of discussion, we assume the organization depicted in Figure 14.6 (*Data Flow, Fetch Cycle*). Four registers are involved:

- **Memory address register (MAR):** Is connected to the address lines of the system bus. It specifies the address in memory for a read or write operation.
- **Memory buffer register (MBR):** Is connected to the data lines of the system bus. It contains the value to be stored in memory or the last value read from memory.

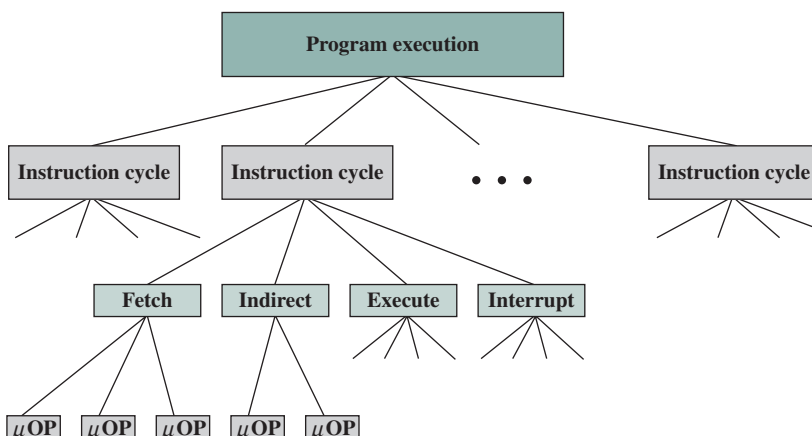

**Figure 20.1** Constituent Elements of a Program Execution


- **Program counter (PC):** Holds the address of the next instruction to be fetched.
- **Instruction register (IR):** Holds the last instruction fetched.

Let us look at the sequence of events for the fetch cycle from the point of view of its effect on the processor registers. An example appears in Figure 20.2. At the beginning of the fetch cycle, the address of the next instruction to be executed is in the program counter (PC); in this case, the address is 1100100. The first step is to move that address to the memory address register (MAR) because this is the only register connected to the address lines of the system bus. The second step is to bring in the instruction. The desired address (in the MAR) is placed on the address bus, the control unit issues a READ command on the control bus, and the result appears on the data bus and is copied into the memory buffer register (MBR). We also need to increment the PC by the instruction length to get ready for the next instruction. Because these two actions (read word from memory, increment PC) do not interfere with each other, we can do them simultaneously to save time. The third step is to move the contents of the MBR to the instruction register (IR). This frees up the MBR for use during a possible indirect cycle.

Thus, the simple fetch cycle actually consists of three steps and four micro-operations. Each micro-operation involves the movement of data into or out of a register. So long as these movements do not interfere with one another, several of them can take place during one step, saving time. Symbolically, we can write this sequence of events as follows:

$$\begin{aligned}
 t_1: \text{MAR} &\leftarrow (\text{PC}) \\
 t_2: \text{MBR} &\leftarrow \text{Memory} \\
 &\text{PC} \leftarrow (\text{PC}) + I \\
 t_3: \text{IR} &\leftarrow (\text{MBR})
 \end{aligned}$$

where  $I$  is the instruction length. We need to make several comments about this sequence. We assume that a clock is available for timing purposes and that it emits regularly spaced clock pulses. Each clock pulse defines a time unit. Thus, all time units are

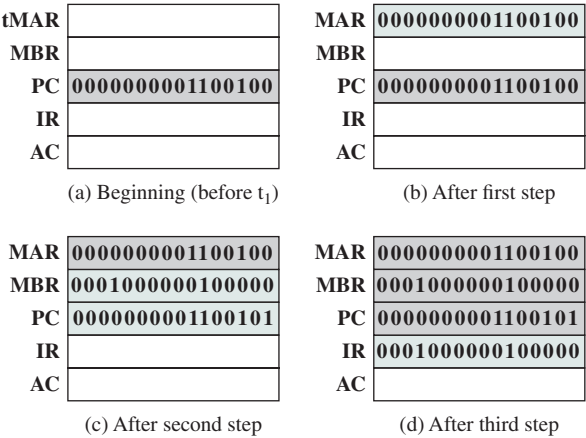

**Figure 20.2** Sequence of Events, Fetch Cycle

of equal duration. Each micro-operation can be performed within the time of a single time unit. The notation ( $t_1, t_2, t_3$ ) represents successive time units. In words, we have

- **First time unit:** Move contents of PC to MAR.
- **Second time unit:** Move contents of memory location specified by MAR to MBR. Increment by  $I$  the contents of the PC.
- **Third time unit:** Move contents of MBR to IR.

Note that the second and third micro-operations both take place during the second time unit. The third micro-operation could have been grouped with the fourth without affecting the fetch operation:

$$\begin{array}{lll} t_1: \text{MAR} & \leftarrow & (\text{PC}) \\ t_2: \text{MBR} & \leftarrow & \text{Memory} \\ t_3: \text{PC} & \leftarrow & (\text{PC}) + I \\ & \text{IR} & \leftarrow (\text{MBR}) \end{array}$$

The groupings of micro-operations must follow two simple rules:

1. The proper sequence of events must be followed. Thus  $(\text{MAR} \leftarrow (\text{PC}))$  must precede  $(\text{MBR} \leftarrow \text{Memory})$  because the memory read operation makes use of the address in the MAR.
2. Conflicts must be avoided. One should not attempt to read to and write from the same register in one time unit, because the results would be unpredictable. For example, the micro-operations  $(\text{MBR} \leftarrow \text{Memory})$  and  $(\text{IR} \leftarrow \text{MBR})$  should not occur during the same time unit.

A final point worth noting is that one of the micro-operations involves an addition. To avoid duplication of circuitry, this addition could be performed by the ALU. The use of the ALU may involve additional micro-operations, depending on the functionality of the ALU and the organization of the processor. We defer a discussion of this point until later in this chapter.

It is useful to compare events described in this and the following subsections to Figure 3.5 (*Example of Program Execution*). Whereas micro-operations are ignored in that figure, this discussion shows the micro-operations needed to perform the subcycles of the instruction cycle.

## The Indirect Cycle

Once an instruction is fetched, the next step is to fetch source operands. Continuing our simple example, let us assume a one-address instruction format, with direct and indirect addressing allowed. If the instruction specifies an indirect address, then an indirect cycle must precede the execute cycle. The data flow differs somewhat from that indicated in Figure 14.7 (*Data Flow, Indirect Cycle*) and includes the following micro-operations:

$$\begin{array}{lll} t_1: \text{MAR} & \leftarrow & (\text{IR}(\text{Address})) \\ t_2: \text{MBR} & \leftarrow & \text{Memory} \\ t_3: \text{IR}(\text{Address}) & \leftarrow & (\text{MBR}(\text{Address})) \end{array}$$

The address field of the instruction is transferred to the MAR. This is then used to fetch the address of the operand. Finally, the address field of the IR is updated from the MBR, so that it now contains a direct rather than an indirect address.

The IR is now in the same state as if indirect addressing had not been used, and it is ready for the execute cycle. We skip that cycle for a moment, to consider the interrupt cycle.

### The Interrupt Cycle

At the completion of the execute cycle, a test is made to determine whether any enabled interrupts have occurred. If so, the interrupt cycle occurs. The nature of this cycle varies greatly from one machine to another. We present a very simple sequence of events, as illustrated in Figure 14.8 (*Data Flow, Indirect Cycle*). We have

```
t1: MBR ← (PC)
t2: MAR ← Save_Address
      PC ← Routine_Address
t3: Memory ← (MBR)
```

In the first step, the contents of the PC are transferred to the MBR, so that they can be saved for return from the interrupt. Then the MAR is loaded with the address at which the contents of the PC are to be saved, and the PC is loaded with the address of the start of the interrupt-processing routine. These two actions may each be a single micro-operation. However, because most processors provide multiple types and/or levels of interrupts, it may take one or more additional micro-operations to obtain the *Save\_Address* and the *Routine\_Address* before they can be transferred to the MAR and PC, respectively. In any case, once this is done, the final step is to store the MBR, which contains the old value of the PC, into memory. The processor is now ready to begin the next instruction cycle.

### The Execute Cycle

The fetch, indirect, and interrupt cycles are simple and predictable. Each involves a small, fixed sequence of micro-operations and, in each case, the same micro-operations are repeated each time around.

This is not true of the execute cycle. Because of the variety of opcodes, there are a number of different sequences of micro-operations that can occur. The control unit examines the opcode and generates a sequence of micro-operations based on the value of the opcode. This is referred to as instruction decoding.

Let us consider several hypothetical examples.

First, consider an add instruction:

```
ADD R1, X
```

which adds the contents of the location X to register R1. The following sequence of micro-operations might occur:

```
t1: MAR ← (IR(address))
t2: MBR ← Memory
t3: R1 ← (R1) + (MBR)
```

We begin with the IR containing the ADD instruction. In the first step, the address portion of the IR is loaded into the MAR. Then the referenced memory location is read. Finally, the contents of R1 and MBR are added by the ALU. Again, this is a simplified example. Additional micro-operations may be required to extract

the register reference from the IR and perhaps to stage the ALU inputs or outputs in some intermediate registers.

Let us look at two more complex examples. A common instruction is increment and skip if zero:

ISZ X

The content of location X is incremented by 1. If the result is 0, the next instruction is skipped. A possible sequence of micro-operations is

```
t1: MAR ← (IR(address))
t2: MBR ← Memory
t3: MBR ← (MBR) + 1
t4: Memory ← (MBR)
    If ((MBR) = 0) then (PC ← (PC) + I)
```

The new feature introduced here is the conditional action. The PC is incremented if (MBR) = 0. This test and action can be implemented as one micro-operation. Note also that this micro-operation can be performed during the same time unit during which the updated value in MBR is stored back to memory.

Finally, consider a subroutine call instruction. As an example, consider a branch-and-save-address instruction:

BSA X

The address of the instruction that follows the BSA instruction is saved in location X, and execution continues at location X + I. The saved address will later be used for return. This is a straightforward technique for supporting subroutine calls. The following micro-operations suffice:

```
t1: MAR ← (IR(address))
    MBR ← (PC)
t2: PC ← (IR(address))
    Memory ← (MBR)
t3: PC ← (PC) + I
```

The address in the PC at the start of the instruction is the address of the next instruction in sequence. This is saved at the address designated in the IR. The latter address is also incremented to provide the address of the instruction for the next instruction cycle.

## The Instruction Cycle

We have seen that each phase of the instruction cycle can be decomposed into a sequence of elementary micro-operations. In our example, there is one sequence each for the fetch, indirect, and interrupt cycles, and, for the execute cycle, there is one sequence of micro-operations for each opcode.

To complete the picture, we need to tie sequences of micro-operations together, and this is done in Figure 20.3. We assume a new 2-bit register called the *instruction cycle code* (ICC). The ICC designates the state of the processor in terms of which portion of the cycle it is in:

00: Fetch  
01: Indirect

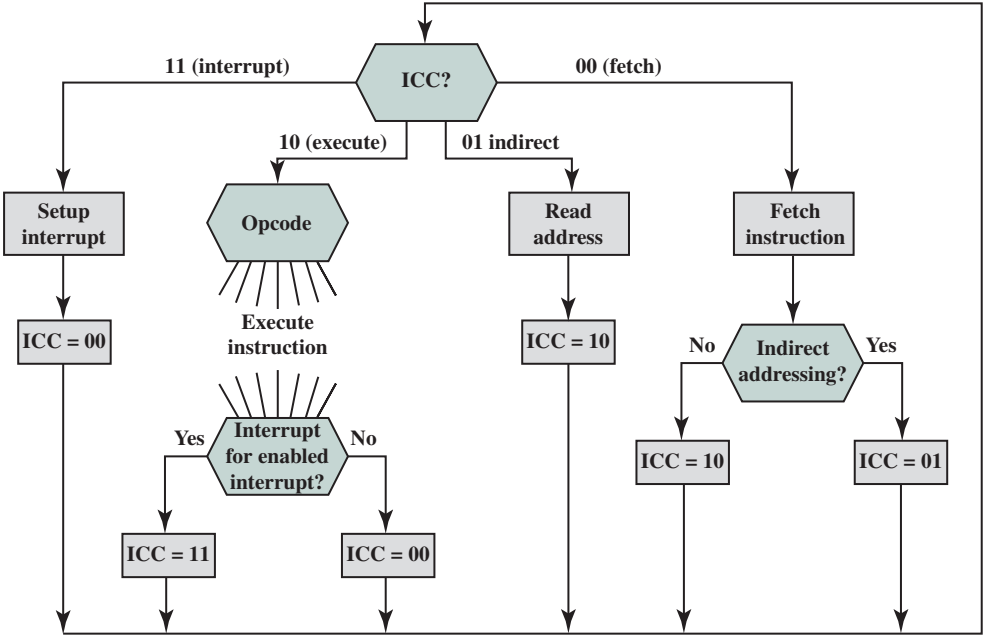


Figure 20.3 Flowchart for Instruction Cycle

10: Execute  
11: Interrupt

At the end of each of the four cycles, the ICC is set appropriately. The indirect cycle is always followed by the execute cycle. The interrupt cycle is always followed by the fetch cycle (see Figure 14.4, *The Instruction Cycle*). For both the fetch and execute cycles, the next cycle depends on the state of the system.

Thus, the flowchart of Figure 20.3 defines the complete sequence of micro-operations, depending only on the instruction sequence and the interrupt pattern. Of course, this is a simplified example. The flowchart for an actual processor would be more complex. In any case, we have reached the point in our discussion in which the operation of the processor is defined as the performance of a sequence of micro-operations. We can now consider how the control unit causes this sequence to occur.

20.2 CONTROL OF THE PROCESSOR

Functional Requirements

As a result of our analysis in the preceding section, we have decomposed the behavior or functioning of the processor into elementary operations, called micro-operations. By reducing the operation of the processor to its most fundamental level, we are able to define exactly what it is that the control unit must cause to happen. Thus, we can define the *functional requirements* for the control unit: those functions that the control unit must perform. A definition of these functional requirements is the basis for the design and implementation of the control unit.



With the information at hand, the following three-step process leads to a characterization of the control unit:

1. Define the basic elements of the processor.
2. Describe the micro-operations that the processor performs.
3. Determine the functions that the control unit must perform to cause the micro-operations to be performed.

We have already performed steps 1 and 2. Let us summarize the results. First, the basic functional elements of the processor are the following:

- ALU
- Registers
- Internal data paths
- External data paths
- Control unit

Some thought should convince you that this is a complete list. The ALU is the functional essence of the computer. Registers are used to store data internal to the processor. Some registers contain status information needed to manage instruction sequencing (e.g., a program status word). Others contain data that go to or come from the ALU, memory, and I/O modules. Internal data paths are used to move data between registers and between register and ALU. External data paths link registers to memory and I/O modules, often by means of a system bus. The control unit causes operations to happen within the processor.

The execution of a program consists of operations involving these processor elements. As we have seen, these operations consist of a sequence of micro-operations. Upon review of Section 20.1, the reader should see that all micro-operations fall into one of the following categories:

- Transfer data from one register to another.
- Transfer data from a register to an external interface (e.g., system bus).
- Transfer data from an external interface to a register.
- Perform an arithmetic or logic operation, using registers for input and output.

All of the micro-operations needed to perform one instruction cycle, including all of the micro-operations to execute every instruction in the instruction set, fall into one of these categories.

We can now be somewhat more explicit about the way in which the control unit functions. The control unit performs two basic tasks:

- **Sequencing:** The control unit causes the processor to step through a series of micro-operations in the proper sequence, based on the program being executed.
- **Execution:** The control unit causes each micro-operation to be performed.

The preceding is a functional description of what the control unit does. The key to how the control unit operates is the use of control signals.

Control Signals

We have defined the elements that make up the processor (ALU, registers, data paths) and the micro-operations that are performed. For the control unit to perform its function, it must have inputs that allow it to determine the state of the system and outputs that allow it to control the behavior of the system. These are the external specifications of the control unit. Internally, the control unit must have the logic required to perform its sequencing and execution functions. We defer a discussion of the internal operation of the control unit to Section 20.3 and Chapter 21. The remainder of this section is concerned with the interaction between the control unit and the other elements of the processor.

Figure 20.4 is a general model of the control unit, showing all of its inputs and outputs. The inputs are:

- **Clock:** This is how the control unit “keeps time.” The control unit causes one micro-operation (or a set of simultaneous micro-operations) to be performed for each clock pulse. This is sometimes referred to as the processor cycle time, or the clock cycle time.
- **Instruction register:** The opcode and addressing mode of the current instruction are used to determine which micro-operations to perform during the execute cycle.
- **Flags:** These are needed by the control unit to determine the status of the processor and the outcome of previous ALU operations. For example, for the increment-and-skip-if-zero (ISZ) instruction, the control unit will increment the PC if the zero flag is set.
- **Control signals from control bus:** The control bus portion of the system bus provides signals to the control unit.

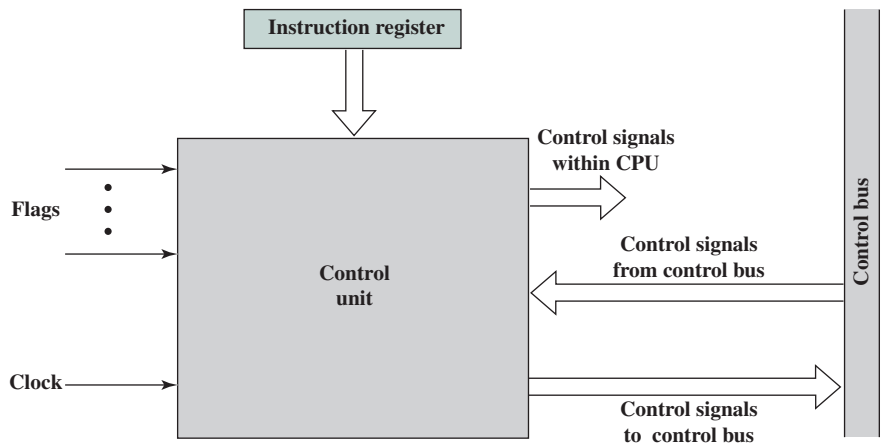


Figure 20.4 Block Diagram of the Control Unit

The outputs are as follows:

- **Control signals within the processor:** These are two types: those that cause data to be moved from one register to another, and those that activate specific ALU functions.
- **Control signals to control bus:** These are also of two types: control signals to memory, and control signals to the I/O modules.

Three types of control signals are used: those that activate an ALU function; those that activate a data path; and those that are signals on the external system bus or other external interface. All of these signals are ultimately applied directly as binary inputs to individual logic gates.

Let us consider again the fetch cycle to see how the control unit maintains control. The control unit keeps track of where it is in the instruction cycle. At a given point, it knows that the fetch cycle is to be performed next. The first step is to transfer the contents of the PC to the MAR. The control unit does this by activating the control signal that opens the gates between the bits of the PC and the bits of the MAR. The next step is to read a word from memory into the MBR and increment the PC. The control unit does this by sending the following control signals simultaneously:

- A control signal that opens gates, allowing the contents of the MAR onto the address bus;
- A memory read control signal on the control bus;
- A control signal that opens the gates, allowing the contents of the data bus to be stored in the MBR;
- Control signals to logic that add 1 to the contents of the PC and store the result back to the PC.


Following this, the control unit sends a control signal that opens gates between the MBR and the IR.

This completes the fetch cycle except for one thing: The control unit must decide whether to perform an indirect cycle or an execute cycle next. To decide this, it examines the IR to see if an indirect memory reference is made.

The indirect and interrupt cycles work similarly. For the execute cycle, the control unit begins by examining the opcode and, on the basis of that, decides which sequence of micro-operations to perform for the execute cycle.

## A Control Signals Example

To illustrate the functioning of the control unit, let us examine a simple example. Figure 20.5 illustrates the example. This is a simple processor with a single accumulator (AC). The data paths between elements are indicated. The control paths for signals emanating from the control unit are not shown, but the terminations of control signals are labeled  $C_i$  and indicated by a circle. The control unit receives inputs from the clock, the IR, and flags. With each clock cycle, the control unit

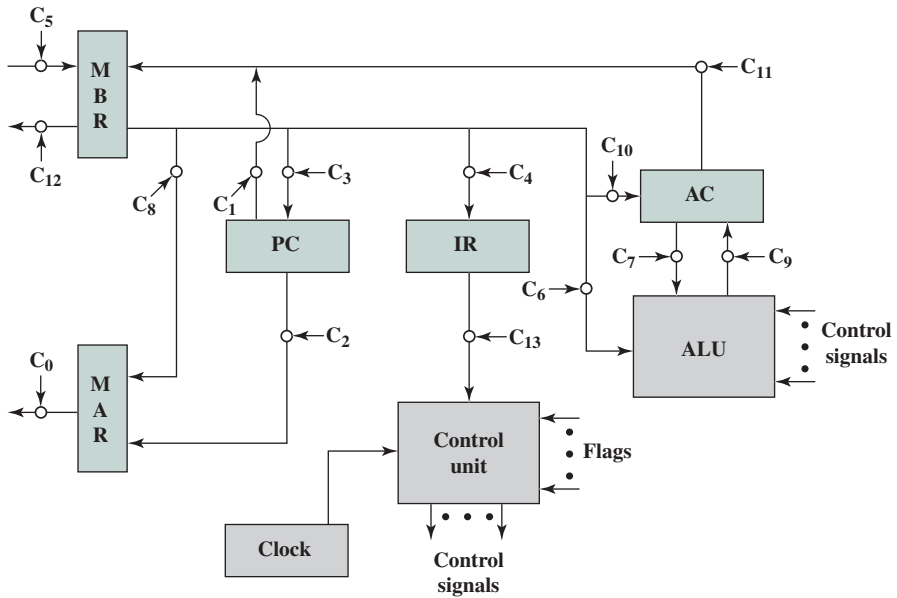

**Figure 20.5** Data Paths and Control Signals

reads all of its inputs and emits a set of control signals. Control signals go to three separate destinations:

- **Data paths:** The control unit controls the internal flow of data. For example, on instruction fetch, the contents of the memory buffer register are transferred to the IR. For each path to be controlled, there is a switch (indicated by a circle in the figure). A control signal from the control unit temporarily opens the gate to let data pass.
- **ALU:** The control unit controls the operation of the ALU by a set of control signals. These signals activate various logic circuits and gates within the ALU.
- **System bus:** The control unit sends control signals out onto the control lines of the system bus (e.g., memory READ).

The control unit must maintain knowledge of where it is in the instruction cycle. Using this knowledge, and by reading all of its inputs, the control unit emits a sequence of control signals that causes micro-operations to occur. It uses the clock pulses to time the sequence of events, allowing time between events for signal levels to stabilize. Table 20.1 indicates the control signals that are needed for some of the micro-operation sequences described earlier. For simplicity, the data and control paths for incrementing the PC and for loading the fixed addresses into the PC and MAR are not shown.

It is worth pondering the minimal nature of the control unit. The control unit is the engine that runs the entire computer. It does this based only on knowing the instructions to be executed and the nature of the results of arithmetic and logical operations (e.g., positive, overflow, etc.). It never gets to see the data being processed or the actual results produced. And it controls everything with a few control signals to points within the processor and a few control signals to the system bus.

**Table 20.1** Micro-operations and Control Signals

	Micro-operations	Active Control Signals
Fetch:	$t_1: \text{MAR} \leftarrow (\text{PC})$	$C_2$
	$t_2: \text{MBR} \leftarrow \text{Memory}$ $\text{PC} \leftarrow (\text{PC}) + 1$	$C_5, C_R$
	$t_3: \text{IR} \leftarrow (\text{MBR})$	$C_4$
Indirect:	$t_1: \text{MAR} \leftarrow (\text{IR}(\text{Address}))$	$C_8$
	$t_2: \text{MBR} \leftarrow \text{Memory}$	$C_5, C_R$
	$t_3: \text{IR}(\text{Address}) \leftarrow (\text{MBR}(\text{Address}))$	$C_4$
Interrupt:	$t_1: \text{MBR} \leftarrow (\text{PC})$	$C_1$
	$t_2: \text{MAR} \leftarrow \text{Save-address}$ $\text{PC} \leftarrow \text{Routine-address}$	
	$t_3: \text{Memory} \leftarrow (\text{MBR})$	$C_{12}, C_W$

$C_R$  = Read control signal to system bus.

$C_W$  = Write control signal to system bus.

## Internal Processor Organization

Figure 20.5 indicates the use of a variety of data paths. The complexity of this type of organization should be clear. More typically, some sort of internal bus arrangement, as was suggested in Figure 14.2 (*Internal Structure of the CPU*), will be used.

Using an internal processor bus, Figure 20.5 can be rearranged as shown in Figure 20.6. A single internal bus connects the ALU and all processor registers. Gates and control signals are provided for movement of data onto and off the bus from each register. Additional control signals control data transfer to and from the system (external) bus and the operation of the ALU.

Two new registers, labeled Y and Z, have been added to the organization. These are needed for the proper operation of the ALU. When an operation involving two operands is performed, one can be obtained from the internal bus, but the other must be obtained from another source. The AC could be used for this purpose, but this limits the flexibility of the system and would not work with a processor with multiple general-purpose registers. Register Y provides temporary storage for the other input. The ALU is a combinatorial circuit (see Chapter 11) with no internal storage. Thus, when control signals activate an ALU function, the input to the ALU is transformed to the output. Therefore, the output of the ALU cannot be directly connected to the bus, because this output would feed back to the input. Register Z provides temporary output storage. With this arrangement, an operation to add a value from memory to the AC would have the following steps:

```

 $t_1: \text{MAR} \leftarrow (\text{IR}(\text{address}))$ 
 $t_2: \text{MBR} \leftarrow \text{Memory}$ 
 $t_3: \text{Y} \leftarrow (\text{MBR})$ 
 $t_4: \text{Z} \leftarrow (\text{AC}) + (\text{Y})$ 
 $t_5: \text{AC} \leftarrow (\text{Z})$ 

```

Other organizations are possible, but, in general, some sort of internal bus or set of internal buses is used. The use of common data paths simplifies the

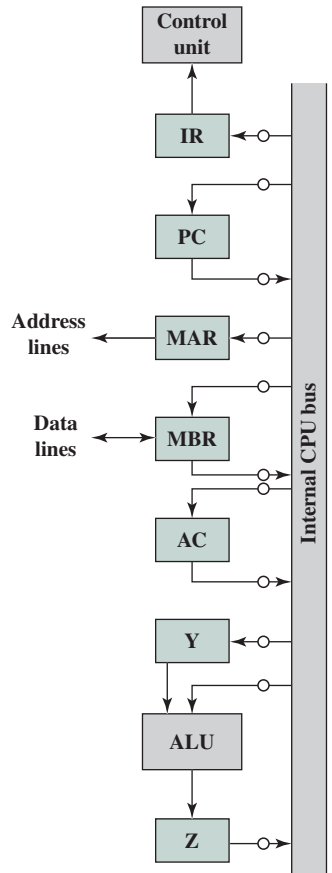


Figure 20.6 CPU with Internal Bus


interconnection layout and the control of the processor. Another practical reason for the use of an internal bus is to save space.

### The Intel 8085

To illustrate some of the concepts introduced thus far in this chapter, let us consider the Intel 8085. Its organization is shown in Figure 20.7. Several key components that may not be self-explanatory are:

- **Incrementer/decrementer address latch:** Logic that can add 1 to or subtract 1 from the contents of the stack pointer or program counter. This saves time by avoiding the use of the ALU for this purpose.
- **Interrupt control:** This module handles multiple levels of interrupt signals.
- **Serial I/O control:** This module interfaces to devices that communicate 1 bit at a time.

Table 20.2 describes the external signals into and out of the 8085. These are linked to the external system bus. These signals are the interface between the 8085 processor and the rest of the system (Figure 20.8).

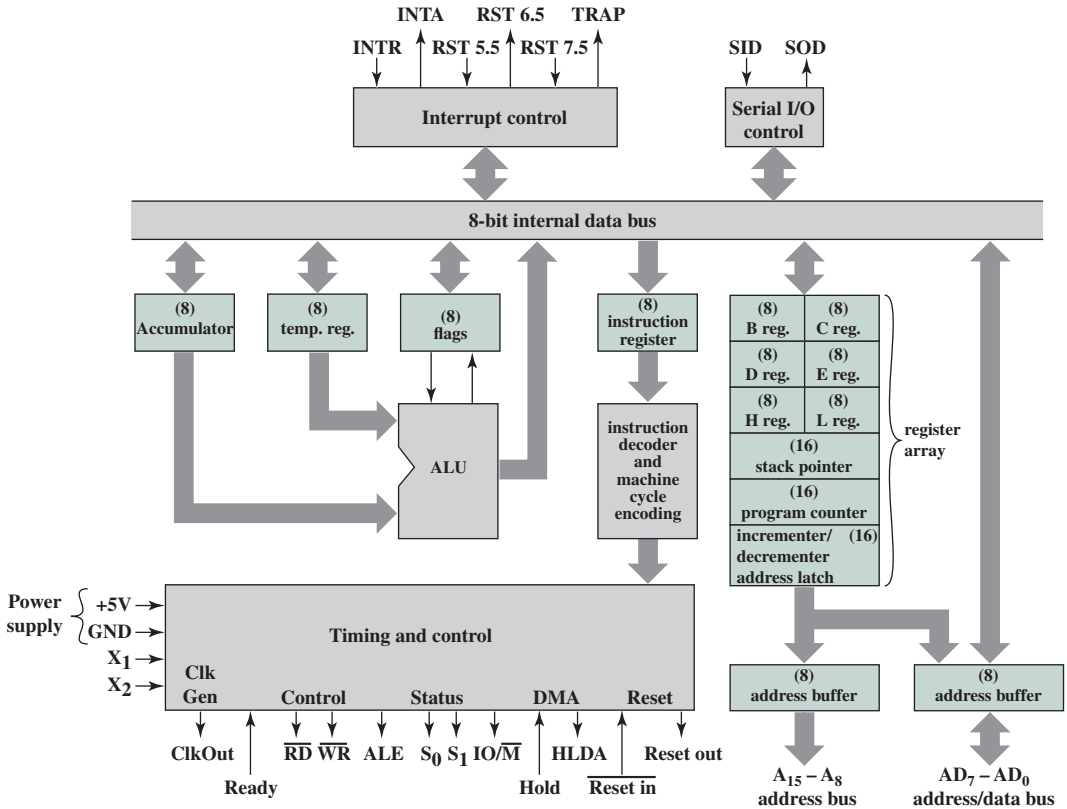

**Figure 20.7** Intel 8085 CPU Block Diagram

The control unit is identified as having two components labeled (1) instruction decoder and machine cycle encoding and (2) timing and control. A discussion of the first component is deferred until the next section. The essence of the control unit is the timing and control module. This module includes a clock and accepts as inputs the current instruction and some external control signals. Its output consists of control signals to the other components of the processor plus control signals to the external system bus.

The timing of processor operations is synchronized by the clock and controlled by the control unit with control signals. Each instruction cycle is divided into from one to five *machine cycles*; each machine cycle is in turn divided into from three to five *states*. Each state lasts one clock cycle. During a state, the processor performs one or a set of simultaneous micro-operations as determined by the control signals.

The number of machine cycles is fixed for a given instruction but varies from one instruction to another. Machine cycles are defined to be equivalent to bus accesses. Thus, the number of machine cycles for an instruction depends on the number of times the processor must communicate with external devices. For example, if an instruction consists of two 8-bit portions, then two machine cycles are required to fetch the instruction. If that instruction involves a 1-byte memory or I/O operation, then a third machine cycle is required for execution.

**Table 20.2**    Intel 8085 External Signals

<i>Address and Data Signals</i>	
<b>High Address (A15–A8)</b>	The high-order 8 bits of a 16-bit address.
<b>Address/Data (AD7–AD0)</b>	The lower-order 8 bits of a 16-bit address or 8 bits of data. This multiplexing saves on pins.
<b>Serial Input Data (SID)</b>	A single-bit input to accommodate devices that transmit serially (one bit at a time).
<b>Serial Output Data (SOD)</b>	A single-bit output to accommodate devices that receive serially.
<i>Timing and Control Signals</i>	
<b>CLK (OUT)</b>	The system clock. The CLK signal goes to peripheral chips and synchronizes their timing.
<b>X1, X2</b>	These signals come from an external crystal or other device to drive the internal clock generator.
<b>Address Latch Enabled (ALE)</b>	Occurs during the first clock state of a machine cycle and causes peripheral chips to store the address lines. This allows the address module (e.g., memory, I/O) to recognize that it is being addressed.
<b>Status (S0, S1)</b>	Control signals used to indicate whether a read or write operation is taking place.
<b>I/O/M</b>	Used to enable either I/O or memory modules for read and write operations.
<b>Read Control (RD)</b>	Indicates that the selected memory or I/O module is to be read and that the data bus is available for data transfer.
<b>Write Control (WR)</b>	Indicates that data on the data bus is to be written into the selected memory or I/O location.
<i>Memory and I/O Initiated Symbols</i>	
<b>Hold</b>	Requests the CPU to relinquish control and use of the external system bus. The CPU will complete execution of the instruction presently in the IR and then enter a hold state, during which no signals are inserted by the CPU to the control, address, or data buses. During the hold state, the bus may be used for DMA operations.
<b>Hold Acknowledge (HOLDA)</b>	This control unit output signal acknowledges the HOLD signal and indicates that the bus is now available.
<b>READY</b>	Used to synchronize the CPU with slower memory or I/O devices. When an addressed device asserts READY, the CPU may proceed with an input (DBIN) or output (WR) operation. Otherwise, the CPU enters a wait state until the device is ready.
<i>Interrupt-Related Signals</i>	
<b>TRAP</b>	Restart Interrupts (RST 7.5, 6.5, 5.5)
<b>Interrupt Request (INTR)</b>	These five lines are used by an external device to interrupt the CPU. The CPU will not honor the request if it is in the hold state or if the interrupt is disabled. An interrupt is honored only at the completion of an instruction. The interrupts are in descending order of priority.
<b>Interrupt Acknowledge</b>	Acknowledges an interrupt.



*CPU Initialization***RESET IN**

Causes the contents of the PC to be set to zero. The CPU resumes execution at location zero.

**RESET OUT**

Acknowledges that the CPU has been reset. The signal can be used to reset the rest of the system.

*Voltage and Ground***VCC**


+5-volt power supply

**VSS**


Electrical ground

Figure 20.9 gives an example of 8085 timing, showing the value of external control signals. Of course, at the same time, the control unit generates internal control signals that control internal data transfers. The diagram shows the instruction cycle for an OUT instruction. Three machine cycles ( $M_1$ ,  $M_2$ ,  $M_3$ ) are needed. During the first, the OUT instruction is fetched. The second machine cycle fetches the second half of the instruction, which contains the number of the I/O device selected for output. During the third cycle, the contents of the AC are written out to the selected device over the data bus.

The Address Latch Enabled (ALE) pulse signals the start of each machine cycle from the control unit. The ALE pulse alerts external circuits. During timing state  $T_1$  of machine cycle  $M_1$ , the control unit sets the IO/M signal to indicate that this is a memory operation. Also, the control unit causes the contents of the PC

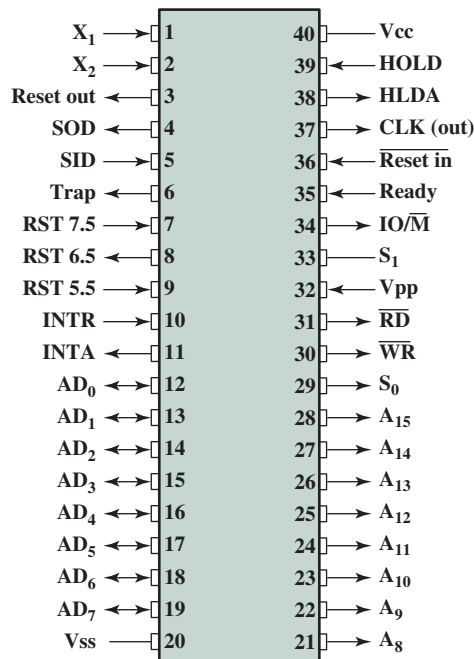

**Figure 20.8** Intel 8085 Pin Configuration

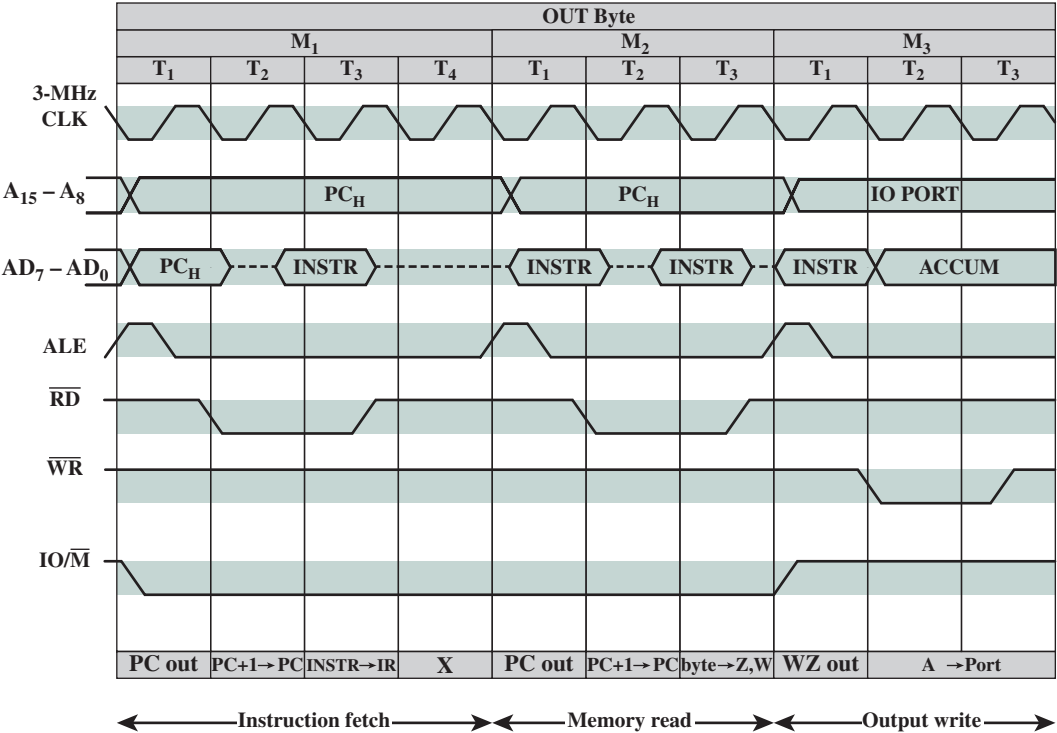

**Figure 20.9** Timing Diagram for Intel 8085 OUT Instruction

to be placed on the address bus (A<sub>15</sub> through A<sub>8</sub>) and the address/data bus (AD<sub>7</sub> through AD<sub>0</sub>). With the falling edge of the ALE pulse, the other modules on the bus store the address.

During timing state T<sub>2</sub>, the addressed memory module places the contents of the addressed memory location on the address/data bus. The control unit sets the Read Control (RD) signal to indicate a read, but it waits until T<sub>3</sub> to copy the data from the bus. This gives the memory module time to put the data on the bus and for the signal levels to stabilize. The final state, T<sub>4</sub>, is a *bus idle* state during which the processor decodes the instruction. The remaining machine cycles proceed in a similar fashion.

### 20.3 HARDWIRED IMPLEMENTATION

We have discussed the control unit in terms of its inputs, output, and functions. We now turn to the topic of control unit implementation. A wide variety of techniques have been used. Most of these fall into one of two categories:

- Hardwired implementation
- Microprogrammed implementation

In a **hardwired implementation**, the control unit is essentially a state machine circuit. Its input logic signals are transformed into a set of output logic signals, which



data paths and through processor circuitry. However, as we have seen, the control unit emits different control signals at different time units within a single instruction cycle. Thus, we would like a counter as input to the control unit, with a different control signal being used for  $T_1, T_2$ , and so forth. At the end of an instruction cycle, the control unit must feed back to the counter to reinitialize it at  $T_1$ .

With these two refinements, the control unit can be depicted as in Figure 20.10.

Control Unit Logic

To define the hardwired implementation of a control unit, all that remains is to discuss the internal logic of the control unit that produces output control signals as a function of its input signals.

Essentially, what must be done is, for each control signal, to derive a Boolean expression of that signal as a function of the inputs. This is best explained by example. Let us consider again our simple example illustrated in Figure 20.5. We saw in Table 20.1 the micro-operation sequences and control signals needed to control three of the four phases of the instruction cycle.

Let us consider a single control signal,  $C_5$ . This signal causes data to be read from the external data bus into the MBR. We can see that it is used twice in Table 20.1. Let us define two new control signals, P and Q, that have the following interpretation:

$PQ = 00$	Fetch Cycle
$PQ = 01$	Indirect Cycle
$PQ = 10$	Execute Cycle
$PQ = 11$	Interrupt Cycle

Then the following Boolean expression defines  $C_5$ :

$$C_5 = \overline{P} \bullet \overline{Q} \bullet T_2 + \overline{P} \bullet Q \bullet T_2$$

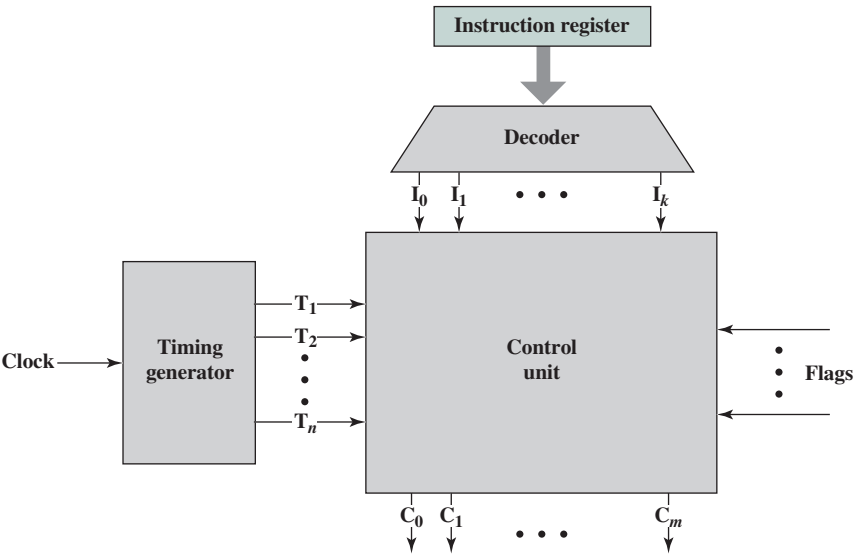


Figure 20.10 Control Unit with Decoded Inputs

That is, the control signal  $C_5$  will be asserted during the second time unit of both the fetch and indirect cycles.

This expression is not complete.  $C_5$  is also needed during the execute cycle. For our simple example, let us assume that there are only three instructions that read from memory: LDA, ADD, and AND. Now we can define  $C_5$  as

$$C_5 = \bar{P} \cdot \bar{Q} \cdot T_2 + \bar{P} \cdot Q \cdot T_2 + P \cdot \bar{Q} \cdot (LDA + ADD + AND) \cdot T_2$$

This same process could be repeated for every control signal generated by the processor. The result would be a set of Boolean equations that define the behavior of the control unit and hence of the processor.

To tie everything together, the control unit must control the state of the instruction cycle. As was mentioned, at the end of each subcycle (fetch, indirect, execute, interrupt), the control unit issues a signal that causes the timing generator to reinitialize and issue  $T_1$ . The control unit must also set the appropriate values of  $P$  and  $Q$  to define the next subcycle to be performed.

The reader should be able to appreciate that in a modern complex processor, the number of Boolean equations needed to define the control unit is very large. The task of implementing a combinatorial circuit that satisfies all of these equations becomes extremely difficult. The result is that a far simpler approach, known as *microprogramming*, is usually used. This is the subject of the next chapter.

## 20.4 KEY TERMS, REVIEW QUESTIONS, AND PROBLEMS

### Key Terms

control bus control path	control signal control unit	hardwired implementation micro-operations
-----------------------------	--------------------------------	--


### Review Questions

- 20.1** Explain the distinction between the written sequence and the time sequence of an instruction.
- 20.2** What is the relationship between instructions and micro-operations?
- 20.3** What is the overall function of a processor's control unit?
- 20.4** Outline a three-step process that leads to a characterization of the control unit.
- 20.5** What basic tasks does a control unit perform?
- 20.6** Provide a typical list of the inputs and outputs of a control unit.
- 20.7** List three types of control signals.
- 20.8** Briefly explain what is meant by a hardwired implementation of a control unit.

### Problems

- 20.1** Your ALU can add its two input registers, and it can logically complement the bits of either input register, but it cannot subtract. Numbers are to be stored in twos complement representation. List the micro-operations your control unit must perform to cause a subtraction.

- 20.2** Show the micro-operations and control signals in the same fashion as Table 20.1 for the processor in Figure 20.5 for the following instructions:
- Load Accumulator
  - Store Accumulator
  - Add to Accumulator
  - AND to Accumulator
  - Jump
  - Jump if  $AC = 0$
  - Complement Accumulator
- 20.3** Assume that propagation delay along the bus and through the ALU of Figure 20.6 are 20 and 100 ns, respectively. The time required for a register to copy data from the bus is 10 ns. What is the time that must be allowed for
- a. data from one register to another?
  - b. the program counter?
- 20.4** Write the sequence of micro-operations required for the bus structure of Figure 20.6 to add a number to the AC when the number is
- a. immediate operand;
  - b. direct-address operand;
  - c. indirect-address operand.
- 20.5** A stack is implemented as shown in Figure 20.11 (see Appendix I for a discussion of stacks). Show the sequence of micro-operations for
- a. popping;
  - b. the stack.

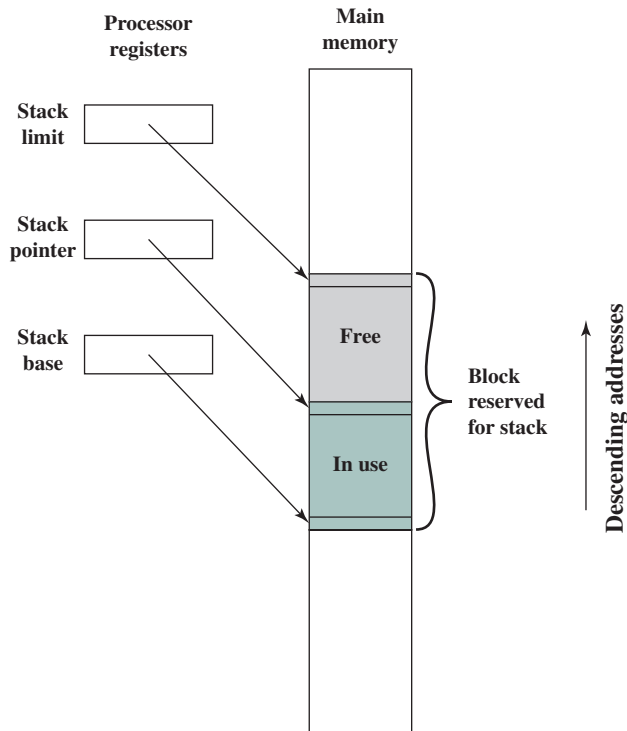

**Figure 20.11** Typical Stack Organization (full/descending)



# CHAPTER

# 21

## MICROPROGRAMMED CONTROL

### **21.1 Basic Concepts**

- Microinstructions
- Microprogrammed Control Unit
- Wilkes Control
- Advantages and Disadvantages

### **21.2 Microinstruction Sequencing**

- Design Considerations
- Sequencing Techniques
- Address Generation
- LSI-11 Microinstruction Sequencing

### **21.3 Microinstruction Execution**

- A Taxonomy of Microinstructions
- Microinstruction Encoding
- LSI-11 Microinstruction Execution
- IBM 3033 Microinstruction Execution

### **21.4 TI 8800**

- Microinstruction Format
- Microsequencer
- Registered ALU

### **21.5 Key Terms, Review Questions, and Problems**

### LEARNING OBJECTIVES

After studying this chapter, you should be able to:

- ◆ Present an overview of the basic concepts of microprogrammed control.
- ◆ Understand the difference between hardwired control and microprogrammed control.
- ◆ Discuss the basic categories of sequencing techniques.
- ◆ Present an overview of the taxonomy of microinstructions.

The term *microprogram* was first coined by M. V. Wilkes in the early 1950s [WILK51]. Wilkes proposed an approach to control unit design that was organized and systematic and avoided the complexities of a hardwired implementation. The idea intrigued many researchers but appeared unworkable because it would require a fast, relatively inexpensive control memory.

The state of the microprogramming art was reviewed by *Datamation* in its February 1964 issue. No microprogrammed system was in wide use at that time, and one of the papers [HILL64] summarized the then-popular view that the future of microprogramming “is somewhat cloudy. None of the major manufacturers has evidenced interest in the technique, although presumably all have examined it.”

This situation changed dramatically within a very few months. IBM’s System/360 was announced in April, and all but the largest models were microprogrammed. Although the 360 series predated the availability of semiconductor ROM, the advantages of microprogramming were compelling enough for IBM to make this move. Microprogramming became a popular technique for implementing the control unit of CISC processors. In recent years, microprogramming has become less used but remains a tool available to computer designers. For example, as we have seen on the Pentium 4, machine instructions are converted into a RISC-like format, most of which are executed without the use of microprogramming. However, some of the instructions are executed using microprogramming.

## 21.1 BASIC CONCEPTS

### Microinstructions

The control unit seems a reasonably simple device. Nevertheless, to implement a control unit as an interconnection of basic logic elements is no easy task. The design must include logic for sequencing through micro-operations, for executing micro-operations, for interpreting opcodes, and for making decisions based on ALU flags. It is difficult to design and test such a piece of hardware. Furthermore, the design is relatively inflexible. For example, it is difficult to change the design if one wishes to add a new machine instruction.

An alternative, which has been used in many CISC processors, is to implement a **microprogrammed control unit**.



Consider Table 21.1. In addition to the use of control signals, each micro-operation is described in symbolic notation. This notation looks suspiciously like a programming language. In fact it is a language, known as a **microprogramming language**. Each line describes a set of micro-operations occurring at one time and is known as a **microinstruction**. A sequence of instructions is known as a **microprogram**, or *firmware*. This latter term reflects the fact that a microprogram is midway between hardware and software. It is easier to design in firmware than hardware, but it is more difficult to write a firmware program than a software program.

How can we use the concept of microprogramming to implement a control unit? Consider that for each micro-operation, all that the control unit is allowed to do is generate a set of control signals. Thus, for any micro-operation, each control line emanating from the control unit is either on or off. This condition can, of course, be represented by a binary digit for each control line. So we could construct a *control word* in which each bit represents one control line. Then each micro-operation would be represented by a different pattern of 1s and 0s in the control word.

Suppose we string together a sequence of control words to represent the sequence of micro-operations performed by the control unit. Next, we must recognize that the sequence of micro-operations is not fixed. Sometimes we have an indirect cycle; sometimes we do not. So let us put our control words in a memory, with each word having a unique address. Now add an address field to each control word, indicating the location of the next control word to be executed if a certain condition is true (e.g., the indirect bit in a memory-reference instruction is 1). Also, add a few bits to specify the condition.

**Table 21.1** Machine Instruction Set for Wilkes Example

Order	Effect of Order
$A\ n$	$C(Acc) + C(n)$ to $Acc_1$
$S\ n$	$C(Acc) - C(n)$ to $Acc_1$
$H\ n$	$C(n)$ to $Acc_2$
$V\ n$	$C(Acc_2) \times C(n)$ to $Acc$ , where $C(n) \geq 0$
$T\ n$	$C(Acc_1)$ to $n$ , 0 to $Acc$
$U\ n$	$C(Acc_1)$ to $n$
$R\ n$	$C(Acc) \times 2^{(n+1)}$ to $Acc$
$L\ n$	$C(Acc) \times 2^{n+1}$ to $Acc$
$G\ n$	IF $C(Acc) < 0$ , transfer control to $n$ ; if $C(Acc) \geq 0$ , ignore (i.e., proceed serially)
$I\ n$	Read next character on input mechanism into $n$
$O\ n$	Send $C(n)$ to output mechanism

*Notation:*  $Acc$  = accumulator

$Acc_1$  = most significant half of accumulator

$Acc_2$  = least significant half of accumulator

$n$  = storage location  $n$


$C(X)$  = contents of  $X$  ( $X$  = register or storage location)

The result is known as a **horizontal microinstruction**, an example of which is shown in Figure 21.1a. The format of the microinstruction or control word is as follows. There is one bit for each internal processor control line and one bit for each system bus control line. There is a condition field indicating the condition under which there should be a branch, and there is a field with the address of the microinstruction to be executed next when a branch is taken. Such a microinstruction is interpreted as follows:


- 1. To execute this microinstruction, turn on all the control lines indicated by a 1 bit; leave off all control lines indicated by a 0 bit. The resulting control signals will cause one or more micro-operations to be performed.
- 2. If the condition indicated by the condition bits is false, execute the next microinstruction in sequence.
- 3. If the condition indicated by the condition bits is true, the next microinstruction to be executed is indicated in the address field.

Figure 21.2 shows how these control words or microinstructions could be arranged in a **control memory**. The microinstructions in each routine are to be executed sequentially. Each routine ends with a branch or jump instruction indicating where to go next. There is a special execute cycle routine whose only purpose is to signify that one of the machine instruction routines (AND, ADD, and so on) is to be executed next, depending on the current opcode.

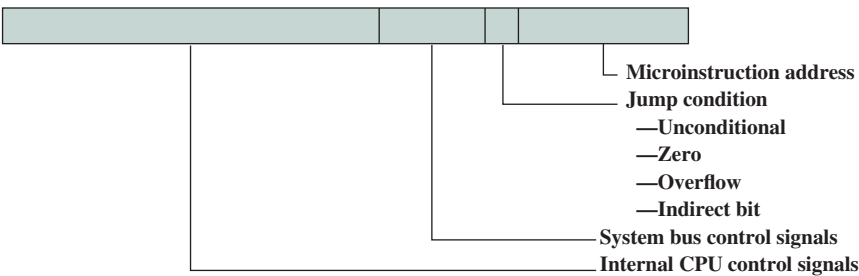The control memory of Figure 21.2 is a concise description of the complete operation of the control unit. It defines the sequence of micro-operations to be




(a) Horizontal microinstruction

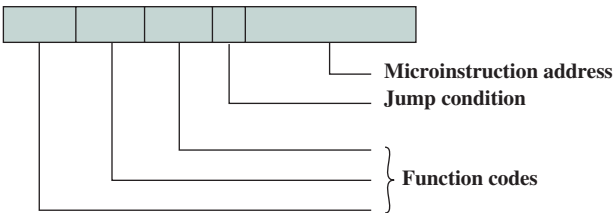

(b) Vertical microinstruction

**Figure 21.1** Typical Microinstruction Formats

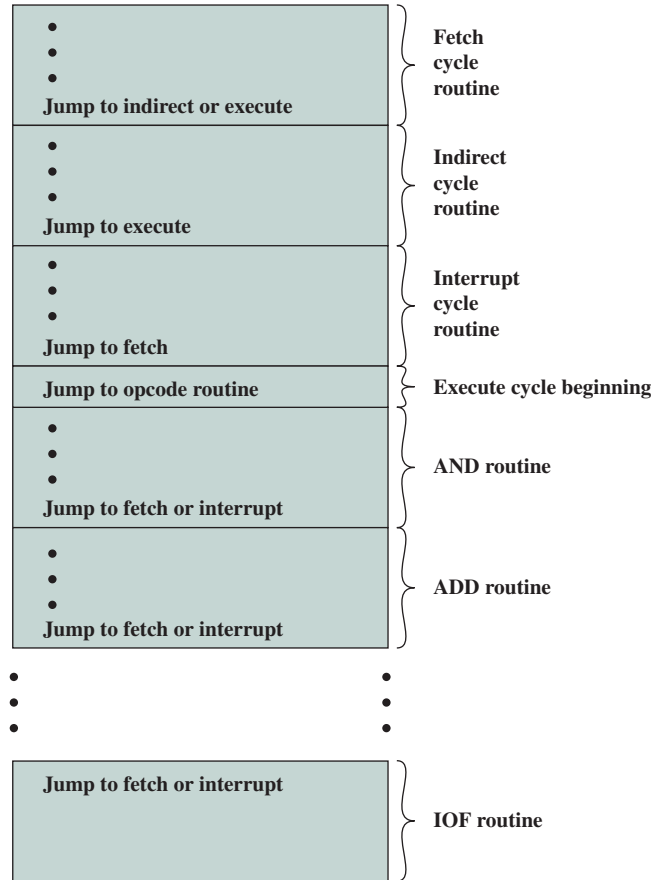


**Figure 21.2** Organization of Control Memory

performed during each cycle (fetch, indirect, execute, interrupt), and it specifies the sequencing of these cycles. If nothing else, this notation would be a useful device for documenting the functioning of a control unit for a particular computer. But it is more than that. It is also a way of implementing the control unit.

### Microprogrammed Control Unit

The control memory of Figure 21.2 contains a program that describes the behavior of the control unit. It follows that we could implement the control unit by simply executing that program.

Figure 21.3 shows the key elements of such an implementation. The set of microinstructions is stored in the *control memory*. The *control address register* contains the address of the next microinstruction to be read. When a microinstruction is read from the control memory, it is transferred to a *control buffer register*. The left-hand portion of that register (see Figure 21.1a) connects to the control lines emanating from the control unit. Thus, *reading* a microinstruction from the control memory is the same as *executing* that microinstruction. The third element shown in the figure is a sequencing unit that loads the control address register and issues a read command.

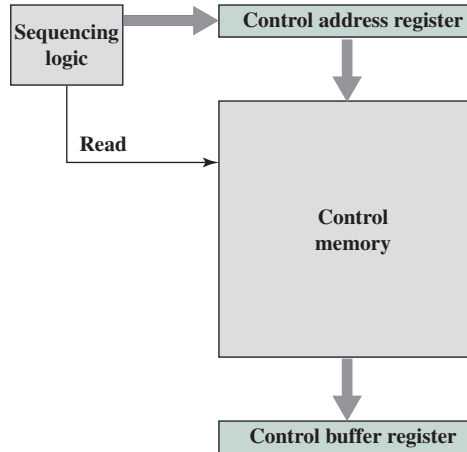

**Figure 21.3** Control Unit Microarchitecture

Let us examine this structure in greater detail, as depicted in Figure 21.4. Comparing this with Figure 21.3, we see that the control unit still has the same inputs (IR, ALU flags, clock) and outputs (control signals). The control unit functions as follows:


1. To execute an instruction, the sequencing logic unit issues a READ command to the control memory.
2. The word whose address is specified in the control address register is read into the control buffer register.
3. The content of the control buffer register generates control signals and next-address information for the sequencing logic unit.
4. The sequencing logic unit loads a new address into the control address register based on the next-address information from the control buffer register and the ALU flags.

All this happens during one clock pulse.

The last step just listed needs elaboration. At the conclusion of each microinstruction, the sequencing logic unit loads a new address into the control address register. Depending on the value of the ALU flags and the control buffer register, one of three decisions is made:

- **Get the next instruction:** Add 1 to the control address register.
- **Jump to a new routine based on a jump microinstruction:** Load the address field of the control buffer register into the control address register.
- **Jump to a machine instruction routine:** Load the control address register based on the opcode in the IR.

Figure 21.4 shows two modules labeled *decoder*. The upper decoder translates the opcode of the IR into a control memory address. The lower decoder is not used for horizontal microinstructions but is used for **vertical microinstructions** (Figure 21.1b). As was mentioned, in a horizontal microinstruction every bit in the

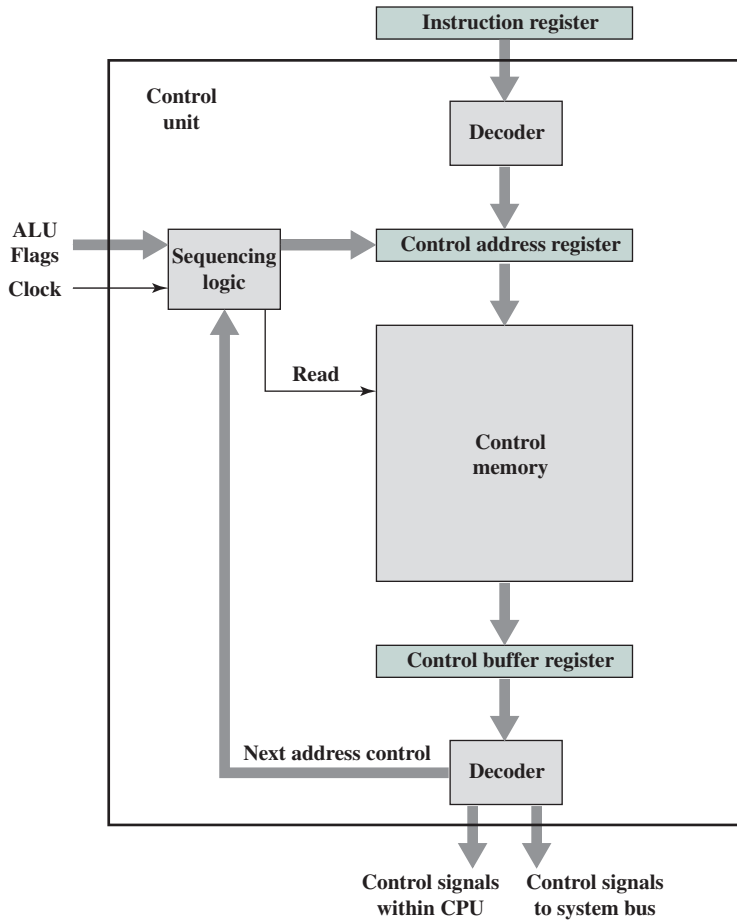


**Figure 21.4** Functioning of Microprogrammed Control Unit

control field attaches to a control line. In a vertical microinstruction, a code is used for each action to be performed [e.g.,  $MAR \leftarrow (PC)$ ], and the decoder translates this code into individual control signals. The advantage of vertical microinstructions is that they are more compact (fewer bits) than horizontal microinstructions, at the expense of a small additional amount of logic and time delay.

### Wilkes Control

As was mentioned, Wilkes first proposed the use of a microprogrammed control unit in 1951 [WILK51]. This proposal was subsequently elaborated into a more detailed design [WILK53]. It is instructive to examine this seminal proposal.

The configuration proposed by Wilkes is depicted in Figure 21.5. The heart of the system is a matrix partially filled with diodes. During a machine cycle, one row of the matrix is activated with a pulse. This generates signals at those points where a diode is present (indicated by a dot in the diagram). The first part of the row generates the control signals that control the operation of the processor. The second part generates the

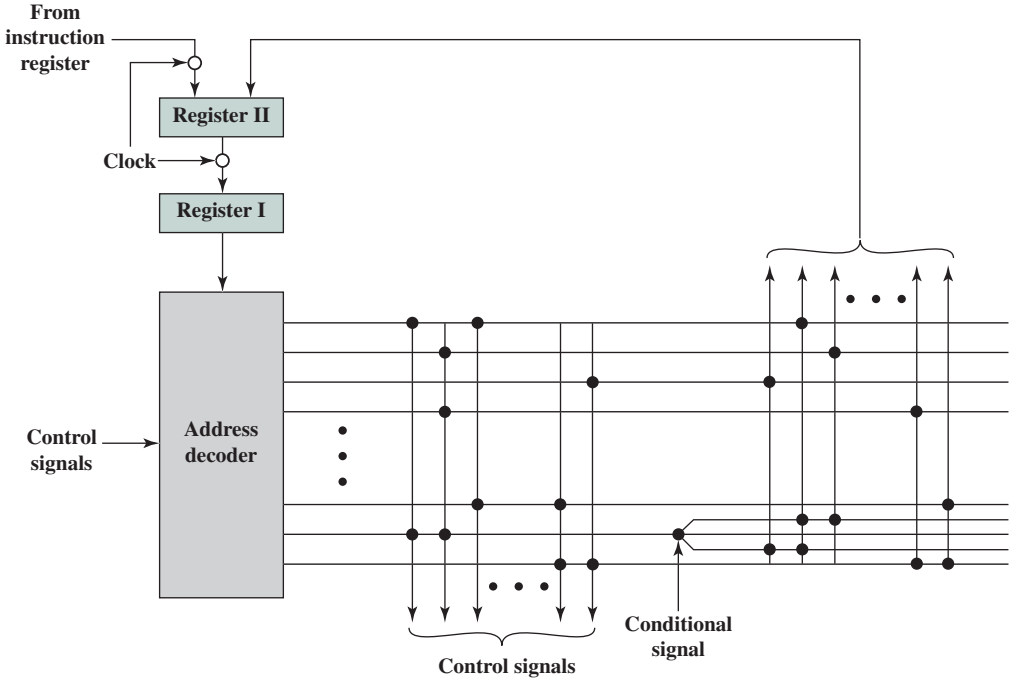

**Figure 21.5** Wilkes's Microprogrammed Control Unit

address of the row to be pulsed in the next machine cycle. Thus, each row of the matrix is one microinstruction, and the layout of the matrix is the control memory.

At the beginning of the cycle, the address of the row to be pulsed is contained in Register I. This address is the input to the decoder, which, when activated by a clock pulse, activates one row of the matrix. Depending on the control signals, either the opcode in the instruction register or the second part of the pulsed row is passed into Register II during the cycle. Register II is then gated to Register I by a clock pulse. Alternating clock pulses are used to activate a row of the matrix and to transfer from Register II to Register I. The two-register arrangement is needed because the decoder is simply a combinatorial circuit; with only one register, the output would become the input during a cycle, causing an unstable condition.

This scheme is very similar to the horizontal microprogramming approach described earlier (Figure 21.1a). The main difference is this: In the previous description, the control address register could be incremented by one to get the next address. In the Wilkes scheme, the next address is contained in the microinstruction. To permit branching, a row must contain two address parts, controlled by a conditional signal (e.g., flag), as shown in the figure.

Having proposed this scheme, Wilkes provides an example of its use to implement the control unit of a simple machine. This example, the first known design of a microprogrammed processor, is worth repeating here because it illustrates many of the contemporary principles of microprogramming.

The processor of the hypothetical machine (the example machine by Wilkes) includes the following registers:

A	Multiplicand
B	Accumulator (least significant half)
C	Accumulator (most significant half)
D	Shift register

In addition, there are three registers and two 1-bit flags accessible only to the control unit. The registers are as follows:

E	Serves as both a memory address register (MAR) and temporary storage
F	Program counter
G	Another temporary register; used for counting

Table 21.1 lists the machine instruction set for this example. Table 21.2 is the complete set of microinstructions, expressed in symbolic form, that implements the control unit. Thus, a total of 38 microinstructions is all that is required to define the system completely.

The first full column gives the address (row number) of each microinstruction. Those addresses corresponding to opcodes are labeled. Thus, when the opcode for the add instruction (A) is encountered, the microinstruction at location 5 is executed. Columns 2 and 3 express the actions to be taken by the ALU and control unit, respectively. Each symbolic expression must be translated into a set of control signals (microinstruction bits). Columns 4 and 5 have to do with the setting and use of the two flags (flip-flops). Column 4 specifies the signal that sets the flag. For example, (1)C<sub>s</sub> means that flag number 1 is set by the sign bit of the number in register C. If column 5 contains a flag identifier, then columns 6 and 7 contain the two alternative microinstruction addresses to be used. Otherwise, column 6 specifies the address of the next microinstruction to be fetched.

Instructions 0 through 4 constitute the fetch cycle. Microinstruction 4 presents the opcode to a decoder, which generates the address of a microinstruction corresponding to the machine instruction to be fetched. The reader should be able to deduce the complete functioning of the control unit from a careful study of Table 21.2.

## Advantages and Disadvantages

The principal advantage of the use of microprogramming to implement a control unit is that it simplifies the design of the control unit. Thus, it is both cheaper and less error prone to implement. A *hardwired* control unit must contain complex logic for sequencing through the many micro-operations of the instruction cycle. On the other hand, the decoders and sequencing logic unit of a microprogrammed control unit are very simple pieces of logic.

The principal disadvantage of a microprogrammed unit is that it will be somewhat slower than a hardwired unit of comparable technology. Despite this, microprogramming is the dominant technique for implementing control units in pure CISC architectures, due to its ease of implementation. RISC processors, with their simpler instruction format, typically use hardwired control units. We now examine the microprogrammed approach in greater detail.

**Table 21.2** Microinstructions for Wilkes Example

Notations:  $A, B, C, \dots$  stand for the various registers in the arithmetical and control register units.  $C$  to  $D$  indicates that the switching circuits connect the output of register  $C$  to the input register  $D$ ;  $(D + A)$  to  $C$  indicates that the output register of  $A$  is connected to the one input of the adding unit (the output of  $D$  is permanently connected to the other input), and the output of the adder to register  $C$ . A numerical symbol  $n$  in quotes (e.g., “ $n$ ”) stands for the source whose output is the number  $n$  in units of the least significant digit.

		Arithmetical Unit	Control Register Unit	Conditional Flip-Flop		Next Microinstruction	
				Set	Use	0	1
	0		$F$ to $G$ and $E$			1	
	1		$(G$ to “1”) to $F$			2	
	2		Store to $G$			3	
	3		$G$ to $E$			4	
	4		$E$ to decoder			—	
$A$	5	$C$ to $D$				16	
$S$	6	$C$ to $D$				17	
$H$	7	Store to $B$				0	
$V$	8	Store to $A$				27	
$T$	9	$C$ to Store				25	
$U$	10	$C$ to Store				0	
$R$	11	$B$ to $D$	$E$ to $G$			19	
$L$	12	$C$ to $D$	$E$ to $G$			22	
$G$	13		$E$ to $G$	$(1)C_5$		18	
$I$	14	Input to Store				0	
$O$	15	Store to Output				0	
	16	$(D + \text{Store})$ to $C$				0	
	17	$(D - \text{Store})$ to $C$				0	
	18				1	0	1
	19	$D$ to $B (R)^*$	$(G - 1)$ to $E$			20	
	20	$C$ to $D$		$(1)E_5$		21	
	21	$D$ to $C (R)$			1	11	0
	22	$D$ to $C (L)^\dagger$	$(G - 1)$ to $E$			23	
	23	$B$ to $D$		$(1)E_5$		24	
	24	$D$ to $B (L)$			1	12	0
	25	“0” to $B$				26	
	26	$B$ to $C$				0	
	27	“0” to $C$	“18” to $E$			28	
	28	$B$ to $D$	$E$ to $G$	$(1)B_1$		29	
	29	$D$ to $B (R)$	$(G - \text{“1”})$ to $E$			30	
	30	$C$ to $D (R)$		$(2)E_5$	1	31	32



		Arithmetical Unit	Control Register Unit	Conditional Flip-Flop		Next Microinstruction	
				Set	Use	0	1
	31	$D$ to $C$			2	28	33
	32	$(D + A)$ to $C$			2	28	33
	33	$B$ to $D$		$(1)B_1$		34	
	34	$D$ to $B$ ( $R$ )				35	
	35	$C$ to $D$ ( $R$ )			1	36	37
	36	$D$ to $C$				0	
	37	$(D - A)$ to $C$				0	

\* Right shift. The switching circuits in the arithmetic unit are arranged so that the least significant digit of the register  $C$  is placed in the most significant place of register  $B$  during right shift micro-operations, and the most significant digit of register  $C$  (sign digit) is repeated (thus making the correction for negative numbers).

† Left shift. The switching circuits are similarly arranged to pass the most significant digit of register  $B$  to the least significant place of register  $C$  during left shift micro-operations.

## 21.2 MICROINSTRUCTION SEQUENCING

The two basic tasks performed by a microprogrammed control unit are as follows:

- **Microinstruction sequencing:** Get the next microinstruction from the control memory.
- **Microinstruction execution:** Generate the control signals needed to execute the microinstruction.

In designing a control unit, these tasks must be considered together, because both affect the format of the microinstruction and the timing of the control unit. In this section, we will focus on sequencing and say as little as possible about format and timing issues. These issues are examined in more detail in the next section.

### Design Considerations

Two concerns are involved in the design of a microinstruction sequencing technique: the size of the microinstruction and the address-generation time. The first concern is obvious; minimizing the size of the control memory reduces the cost of that component. The second concern is simply a desire to execute microinstructions as fast as possible.

In executing a microprogram, the address of the next microinstruction to be executed is in one of these categories:

- Determined by instruction register
- Next sequential address
- Branch

The first category occurs only once per instruction cycle, just after an instruction is fetched. The second category is the most common in most designs. However, the design cannot be optimized just for sequential access. Branches, both conditional and unconditional, are a necessary part of a microprogram. Furthermore, microinstruction sequences tend to be short; one out of every three or four microinstructions could be a branch [SIEW82]. Thus, it is important to design compact, time-efficient techniques for microinstruction branching.

Sequencing Techniques

Based on the current microinstruction, condition flags, and the contents of the instruction register, a control memory address must be generated for the next microinstruction. A wide variety of techniques have been used. We can group them into three general categories, as illustrated in Figures 21.6 to 21.8. These categories are based on the format of the address information in the microinstruction:


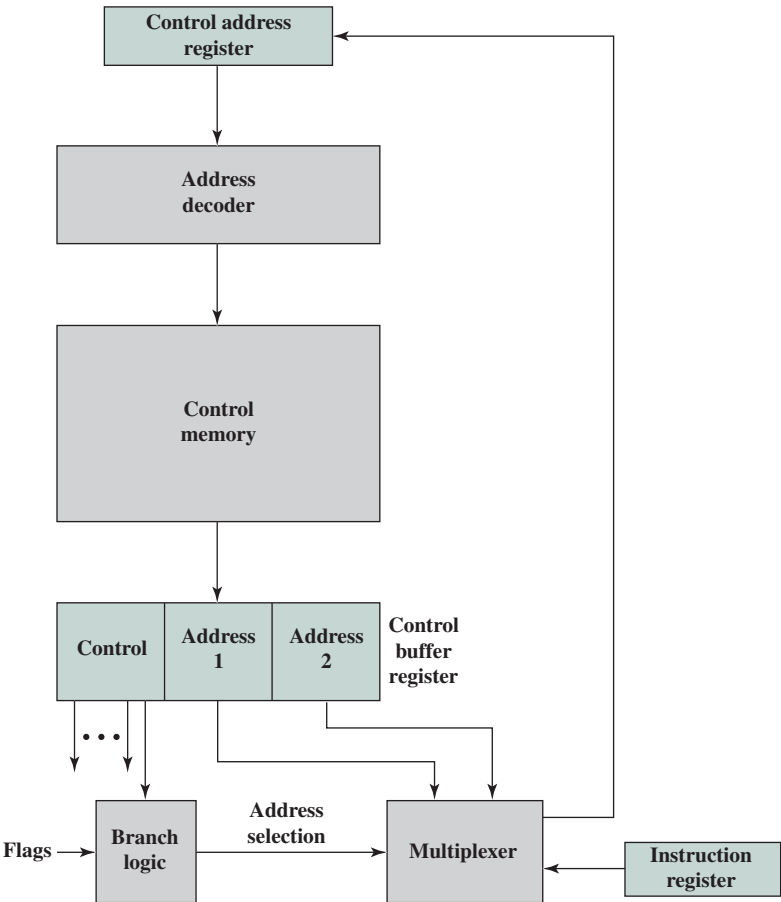


Figure 21.6 Branch Control Logic: Two Address Fields

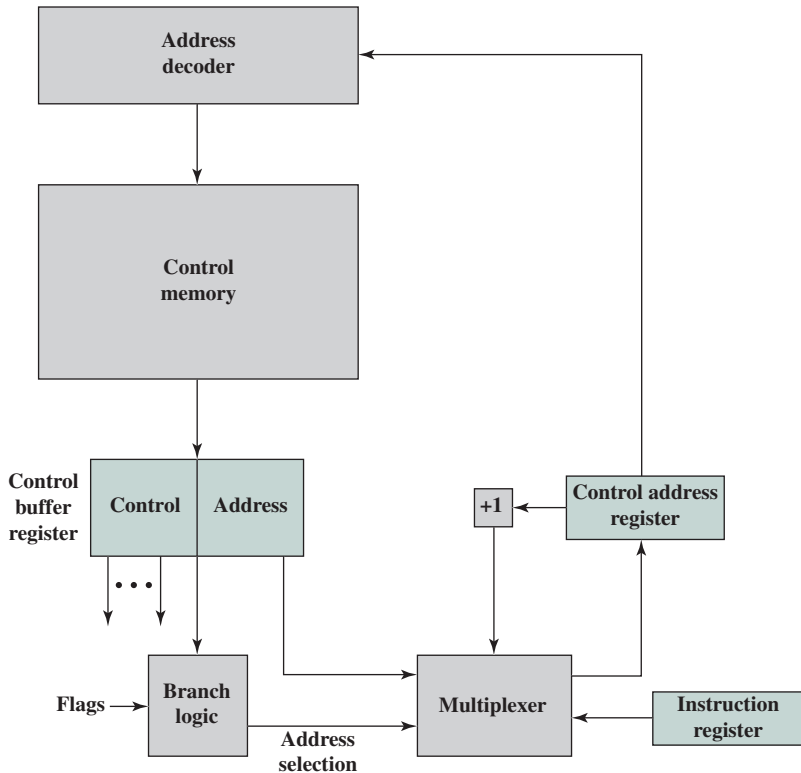


**Figure 21.7** Branch Control Logic: Single Address Field

- Two address fields
- Single address field
- Variable format

The simplest approach is to provide two address fields in each microinstruction. Figure 21.6 suggests how this information is to be used. A multiplexer is provided that serves as a destination for both address fields plus the instruction register. Based on an address-selection input, the multiplexer transmits either the opcode or one of the two addresses to the control address register (CAR). The CAR is subsequently decoded to produce the next microinstruction address. The address-selection signals are provided by a branch logic module whose input consists of control unit flags plus bits from the control portion of the microinstruction.

Although the two-address approach is simple, it requires more bits in the microinstruction than other approaches. With some additional logic, savings can be achieved. A common approach is to have a single address field (Figure 21.7). With this approach, the options for next address are as follows:

- Address field
- Instruction register code
- Next sequential address

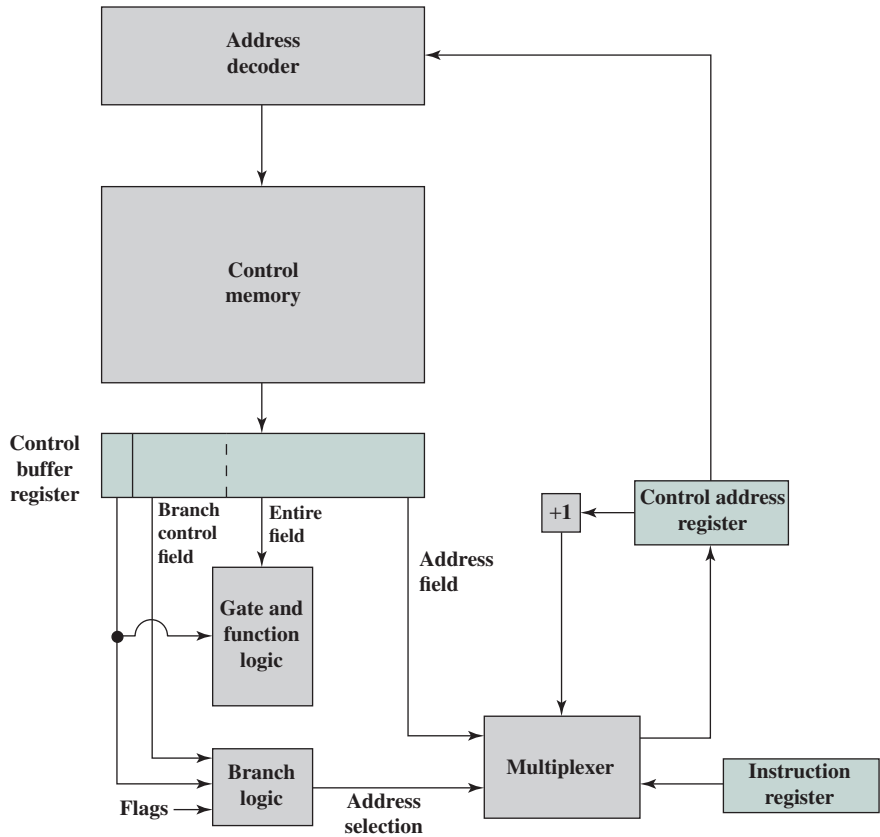

**Figure 21.8** Branch Control Logic: Variable Format

The address-selection signals determine which option is selected. This approach reduces the number of address fields to one. Note, however, that the address field often will not be used. Thus, there is some inefficiency in the microinstruction coding scheme.

Another approach is to provide for two entirely different microinstruction formats (Figure 21.8). One bit designates which format is being used. In one format, the remaining bits are used to activate control signals. In the other format, some bits drive the branch logic module, and the remaining bits provide the address. With the first format, the next address is either the next sequential address or an address derived from the instruction register. With the second format, either a conditional or unconditional branch is being specified. One disadvantage of this approach is that one entire cycle is consumed with each branch microinstruction. With the other approaches, address generation occurs as part of the same cycle as control signal generation, minimizing control memory accesses.

The approaches just described are general. Specific implementations will often involve a variation or combination of these techniques.

## Address Generation

We have looked at the sequencing problem from the point of view of format considerations and general logic requirements. Another viewpoint is to consider the various ways in which the next address can be derived or computed.

Table 21.3 lists the various address generation techniques. These can be divided into explicit techniques, in which the address is explicitly available in the microinstruction, and implicit techniques, which require additional logic to generate the address.

We have essentially dealt with the explicit techniques. With a two-field approach, two alternative addresses are available with each microinstruction. Using either a single address field or a variable format, various branch instructions can be implemented. A conditional branch instruction depends on the following types of information:

- ALU flags
- Part of the opcode or address mode fields of the machine instruction
- Parts of a selected register, such as the sign bit
- Status bits within the control unit


Several implicit techniques are also commonly used. One of these, mapping, is required with virtually all designs. The opcode portion of a machine instruction must be mapped into a microinstruction address. This occurs only once per instruction cycle.

A common implicit technique is one that involves combining or adding two portions of an address to form the complete address. This approach was taken for the IBM S/360 family [TUCK67] and used on many of the S/370 models. We will use the IBM 3033 as an example.

The control address register on the IBM 3033 is 13 bits long and is illustrated in Figure 21.9. Two parts of the address can be distinguished. The highest-order 8 bits (00–07) normally do not change from one microinstruction cycle to the next. During the execution of a microinstruction, these 8 bits are copied directly from an 8-bit field of the microinstruction (the BA field) into the highest-order 8 bits of the control address register. This defines a block of 32 microinstructions in control memory. The remaining 5 bits of the control address register are set to specify the specific address of the microinstruction to be fetched next. Each of these bits is determined by a 4-bit field (except one is a 7-bit field) in the current microinstruction; the field specifies the condition for setting the corresponding bit. For example, a bit in the control address register might be set to 1 or 0 depending on whether a carry occurred on the last ALU operation.

**Table 21.3** Microinstruction Address Generation Techniques

Explicit	Implicit
Two-field	Mapping
Unconditional branch	Addition
Conditional branch	Residual control

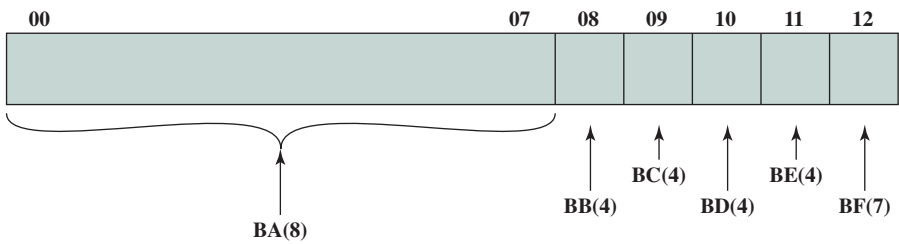

**Figure 21.9** IBM 3033 Control Address Register

The final approach listed in Table 21.3 is termed *residual control*. This approach involves the use of a microinstruction address that has previously been saved in temporary storage within the control unit. For example, some microinstruction sets come equipped with a subroutine facility. An internal register or stack of registers is used to hold return addresses. An example of this approach is taken on the LSI-11, which we now examine.

### LSI-11 Microinstruction Sequencing

The LSI-11 is a microcomputer version of a PDP-11, with the main components of the system residing on a single board. The LSI-11 is implemented using a microprogrammed control unit [SEBE76].

The LSI-11 makes use of a 22-bit microinstruction and a control memory of 2K 22-bit words. The next microinstruction address is determined in one of five ways:

- **Next sequential address:** In the absence of other instructions, the control unit's control address register is incremented by 1.
- **Opcode mapping:** At the beginning of each instruction cycle, the next microinstruction address is determined by the opcode.
- **Subroutine facility:** Explained presently.
- **Interrupt testing:** Certain microinstructions specify a test for interrupts. If an interrupt has occurred, this determines the next microinstruction address.
- **Branch:** Conditional and unconditional branch microinstructions are used.

A one-level subroutine facility is provided. One bit in every microinstruction is dedicated to this task. When the bit is set, an 11-bit return register is loaded with the updated contents of the control address register. A subsequent microinstruction that specifies a return will cause the control address register to be loaded from the return register.

The return is one form of unconditional branch instruction. Another form of unconditional branch causes the bits of the control address register to be loaded from 11 bits of the microinstruction. The conditional branch instruction makes use of a 4-bit test code within the microinstruction. This code specifies testing of various ALU condition codes to determine the branch decision. If the condition is not true, the next sequential address is selected. If it is true, the 8 lowest-order bits of the control address register are loaded from 8 bits of the microinstruction. This allows branching within a 256-word page of memory.

As can be seen, the LSI-11 includes a powerful address sequencing facility within the control unit. This allows the microprogrammer considerable flexibility and can ease the microprogramming task. On the other hand, this approach requires more control unit logic than do simpler capabilities.

## 21.3 MICROINSTRUCTION EXECUTION

The microinstruction cycle is the basic event on a microprogrammed processor. Each cycle is made up of two parts: fetch and execute. The fetch portion is determined by the generation of a microinstruction address, and this was dealt with in the preceding section. This section deals with the execution of a microinstruction.

Recall that the effect of the execution of a microinstruction is to generate control signals. Some of these signals control points internal to the processor. The remaining signals go to the external control bus or other external interface. As an incidental function, the address of the next microinstruction is determined.

The preceding description suggests the organization of a control unit shown in Figure 21.10. This slightly revised version of Figure 21.4 emphasizes the focus of this section. The major modules in this diagram should by now be clear. The sequencing logic module contains the logic to perform the functions discussed in the preceding section. It generates the address of the next microinstruction, using as inputs the instruction register, ALU flags, the control address register (for incrementing), and the control buffer register. The last may provide an actual address, control bits, or both. The module is driven by a clock that determines the timing of the microinstruction cycle.

The control logic module generates control signals as a function of some of the bits in the microinstruction. It should be clear that the format and content of the microinstruction determines the complexity of the control logic module.


### A Taxonomy of Microinstructions

Microinstructions can be classified in a variety of ways. Distinctions that are commonly made in the literature include the following:

- Vertical/horizontal
- Packed/unpacked
- Hard/soft microprogramming
- Direct/indirect encoding

All of these bear on the format of the microinstruction. None of these terms has been used in a consistent, precise way in the literature. However, an examination of these pairs of qualities serves to illuminate microinstruction design alternatives. In the following paragraphs, we first look at the key design issue underlying all of these pairs of characteristics, and then we look at the concepts suggested by each pair.

In the original proposal by Wilkes [WILK51], each bit of a microinstruction either directly produced a control signal or directly produced one bit of the next address. We have seen, in the preceding section, that more complex address

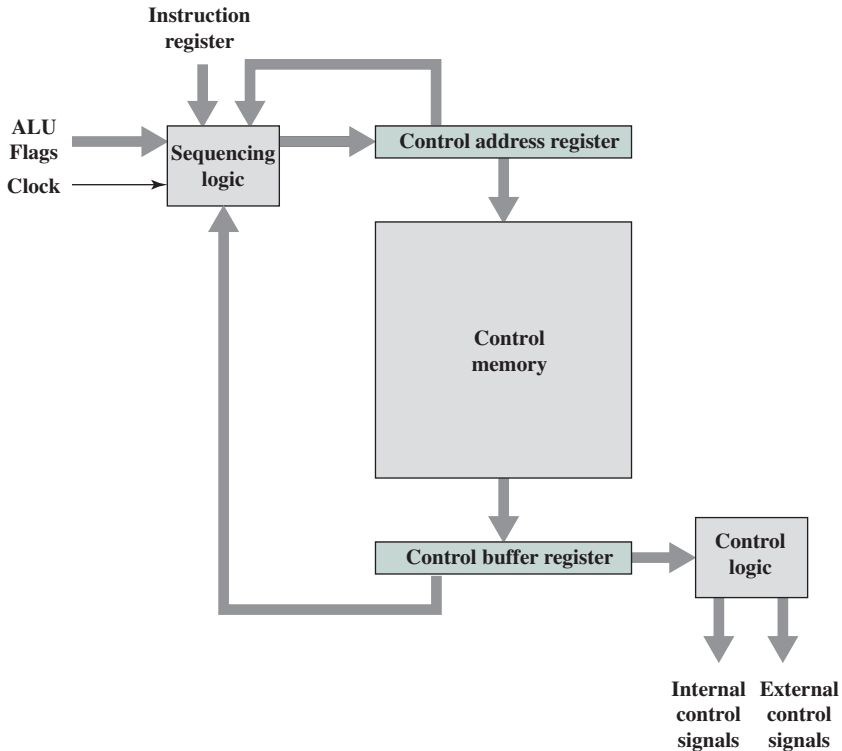

**Figure 21.10** Control Unit Organization

sequencing schemes, using fewer microinstruction bits, are possible. These schemes require a more complex sequencing logic module. A similar sort of trade-off exists for the portion of the microinstruction concerned with control signals. By encoding control information, and subsequently decoding it to produce control signals, control word bits can be saved.

How can this encoding be done? To answer that, consider that there are a total of  $K$  different internal and external control signals to be driven by the control unit. In Wilkes's scheme,  $K$  bits of the microinstruction would be dedicated to this purpose. This allows all of the  $2K$  possible combinations of control signals to be generated during any instruction cycle. But we can do better than this if we observe that not all of the possible combinations will be used. Examples include the following:

- Two sources cannot be gated to the same destination (e.g.,  $C_2$  and  $C_8$  in Figure 21.5).
- A register cannot be both source and destination (e.g.,  $C_5$  and  $C_{12}$  in Figure 21.5).
- Only one pattern of control signals can be presented to the ALU at a time.
- Only one pattern of control signals can be presented to the external control bus at a time.



So, for a given processor, all possible allowable combinations of control signals could be listed, giving some number  $Q < 2^K$  possibilities. These could be encoded with a minimum  $\log_2 Q$  bits, with  $(\log_2 Q) < K$ . This would be the tightest possible form of encoding that preserves all allowable combinations of control signals. In practice, this form of encoding is not used, for two reasons:

- It is as difficult to program as a pure decoded (Wilkes) scheme. This point is discussed further presently.
- It requires a complex and therefore slow control logic module.

Instead, some compromises are made. These are of two kinds:

- More bits than are strictly necessary are used to encode the possible combinations.
- Some combinations that are physically allowable are not possible to encode.

The latter kind of compromise has the effect of reducing the number of bits. The net result, however, is to use more than  $\log_2 Q$  bits.

In the next subsection, we will discuss specific encoding techniques. The remainder of this subsection deals with the effects of encoding and the various terms used to describe it.

Based on the preceding, we can see that the control signal portion of the microinstruction format falls on a spectrum. At one extreme, there is one bit for each control signal; at the other extreme, a highly encoded format is used. Table 21.4 shows that other characteristics of a microprogrammed control unit also fall along a spectrum and that these spectra are, by and large, determined by the degree-of-encoding spectrum.

The second pair of items in the table is rather obvious. The pure Wilkes scheme will require the most bits. It should also be apparent that this extreme presents the most detailed view of the hardware. Every control signal is individually controllable

**Table 21.4** The Microinstruction Spectrum

Characteristics	
Unencoded	Highly encoded
Many bits	Few bits
Detailed view of hardware	Aggregated view of hardware
Difficult to program	Easy to program
Concurrency fully exploited	Concurrency not fully exploited
Little or no control logic	Complex control logic
Fast execution	Slow execution
Optimize performance	Optimize programming
Terminology	
Unpacked	Packed
Horizontal	Vertical
Hard	Soft

by the microprogrammer. Encoding is done in such a way as to aggregate functions or resources, so that the microprogrammer is viewing the processor at a higher, less detailed level. Furthermore, the encoding is designed to ease the microprogramming burden. Again, it should be clear that the task of understanding and orchestrating the use of all the control signals is a difficult one. As was mentioned, one of the consequences of encoding, typically, is to prevent the use of certain otherwise allowable combinations.

The preceding paragraph discusses microinstruction design from the microprogrammer's point of view. But the degree of encoding also can be viewed from its hardware effects. With a pure unencoded format, little or no decode logic is needed; each bit generates a particular control signal. As more compact and more aggregated encoding schemes are used, more complex decode logic is needed. This, in turn, may affect performance. More time is needed to propagate signals through the gates of the more complex control logic module. Thus, the execution of encoded microinstructions takes longer than the execution of unencoded ones.

Therefore, all of the characteristics listed in Table 21.4 fall along a spectrum of design strategies. In general, a design that falls toward the left end of the spectrum is intended to optimize the performance of the control unit. Designs toward the right end are more concerned with optimizing the process of microprogramming. Indeed, microinstruction sets near the right end of the spectrum look very much like machine instruction sets. A good example of this is the LSI-11 design, described later in this section. Typically, when the objective is simply to implement a control unit, the design will be near the left end of the spectrum. The IBM 3033 design, discussed presently, is in this category. As we shall discuss later, some systems permit a variety of users to construct different microprograms using the same microinstruction facility. In the latter cases, the design is likely to fall near the right end of the spectrum.

We can now deal with some of the terminology introduced earlier. Table 21.4 indicates how three of these pairs of terms relate to the microinstruction spectrum. In essence, all of these pairs describe the same thing but emphasize different design characteristics.

The degree of packing relates to the degree of identification between a given control task and specific microinstruction bits. As the bits become more *packed*, a given number of bits contains more information. Thus, packing connotes encoding. The terms *horizontal* and *vertical* relate to the relative width of microinstructions. [SIEW82] suggests as a rule of thumb that vertical microinstructions have lengths in the range of 16 to 40 bits and that horizontal microinstructions have lengths in the range of 40 to 100 bits. The terms *hard* and *soft* microprogramming are used to suggest the degree of closeness to the underlying control signals and hardware layout. Hard microprograms are generally fixed and committed to read-only memory. Soft microprograms are more changeable and are suggestive of user microprogramming.

The other pair of terms mentioned at the beginning of this subsection refers to direct versus indirect encoding, a subject to which we now turn.


### Microinstruction Encoding

In practice, microprogrammed control units are not designed using a pure unencoded or horizontal microinstruction format. At least some degree of encoding is used to reduce control memory width and to simplify the task of microprogramming.


The basic technique for encoding is illustrated in Figure 21.11a. The microinstruction is organized as a set of fields. Each field contains a code, which, upon decoding, activates one or more control signals.

Let us consider the implications of this layout. When the microinstruction is executed, every field is decoded and generates control signals. Thus, with  $N$  fields,  $N$  simultaneous actions are specified. Each action results in the activation of one or more control signals. Generally, but not always, we will want to design the format so that each control signal is activated by no more than one field. Clearly, however, it must be possible for each control signal to be activated by at least one field.

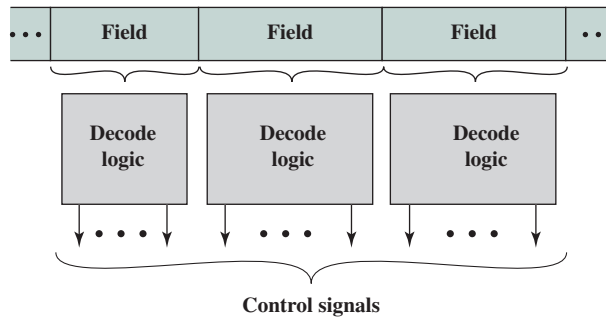Now consider the individual field. A field consisting of  $L$  bits can contain one of  $2^L$  codes, each of which can be encoded to a different control signal pattern. Because only one code can appear in a field at a time, the codes are mutually exclusive, and, therefore, the actions they cause are mutually exclusive.



(a) Direct encoding

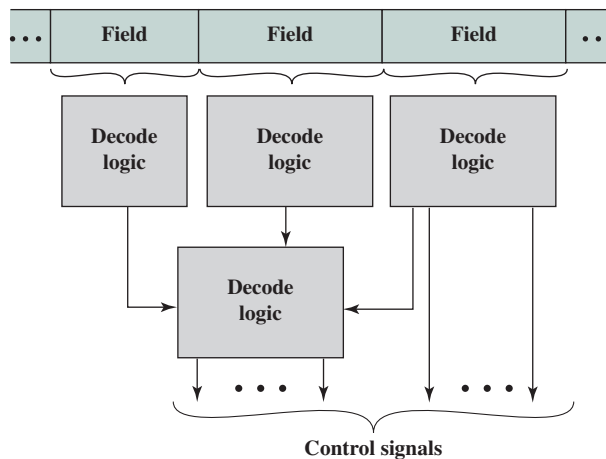

(b) Indirect encoding


**Figure 21.11** Microinstruction Encoding

The design of an encoded microinstruction format can now be stated in simple terms:


- Organize the format into independent fields. That is, each field depicts a set of actions (pattern of control signals) such that actions from different fields can occur simultaneously.
- Define each field such that the alternative actions that can be specified by the field are mutually exclusive. That is, only one of the actions specified for a given field could occur at a time.

Two approaches can be taken for organizing the encoded microinstruction into fields: functional and resource. The *functional encoding* method identifies functions within the machine and designates fields by function type. For example, if various sources can be used for transferring data to the accumulator, one field can be designated for this purpose, with each code specifying a different source. *Resource encoding* views the machine as consisting of a set of independent resources and devotes one field to each (e.g., I/O, memory, ALU).

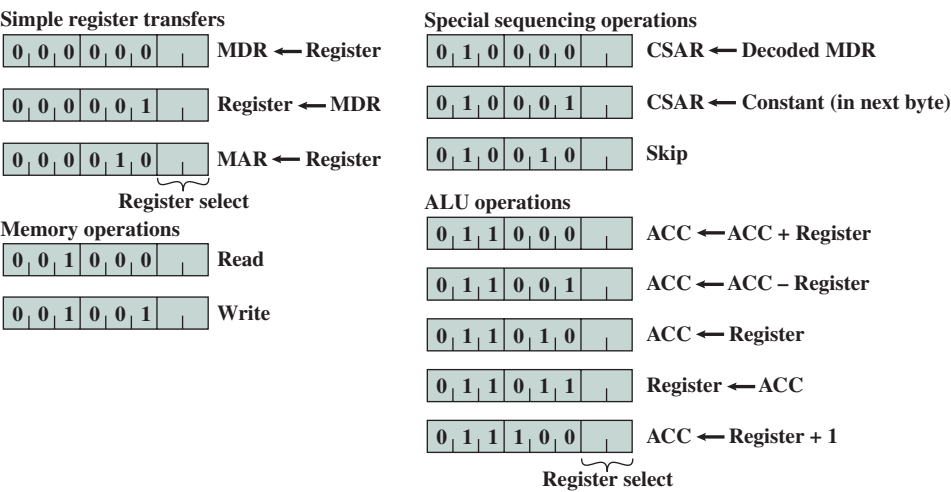Another aspect of encoding is whether it is direct or indirect (Figure 21.11b). With indirect encoding, one field is used to determine the interpretation of another



(a) Vertical microinstruction format

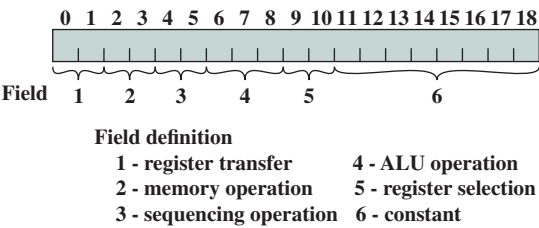

(b) Horizontal microinstruction format

**Figure 21.12** Alternative Microinstruction Formats for a Simple Machine

field. For example, consider an ALU that is capable of performing eight different arithmetic operations and eight different shift operations. A 1-bit field could be used to indicate whether a shift or arithmetic operation is to be used; a 3-bit field would indicate the operation. This technique generally implies two levels of decoding, increasing propagation delays.


Figure 21.12 is a simple example of these concepts. Assume a processor with a single accumulator and several internal registers, such as a program counter and a temporary register for ALU input. Figure 21.12a shows a highly vertical format. The first 3 bits indicate the type of operation, the next 3 encode the operation, and the final 2 select an internal register. Figure 21.12b is a more horizontal approach, although encoding is still used. In this case, different functions appear in different fields.

### LSI-11 Microinstruction Execution

The LSI-11 [SEBE76] is a good example of a vertical microinstruction approach. We look first at the organization of the control unit, then at the microinstruction format.

**LSI-11 CONTROL UNIT ORGANIZATION** The LSI-11 is the first member of the PDP-11 family that was offered as a single-board processor. The board contains three LSI chips, an internal bus known as the *microinstruction bus* (MIB), and some additional interfacing logic.

Figure 21.13 depicts, in simplified form, the organization of the LSI-11 processor. The three chips are the data, control, and control store chips. The data chip contains an 8-bit ALU, twenty-six 8-bit registers, and storage for several condition

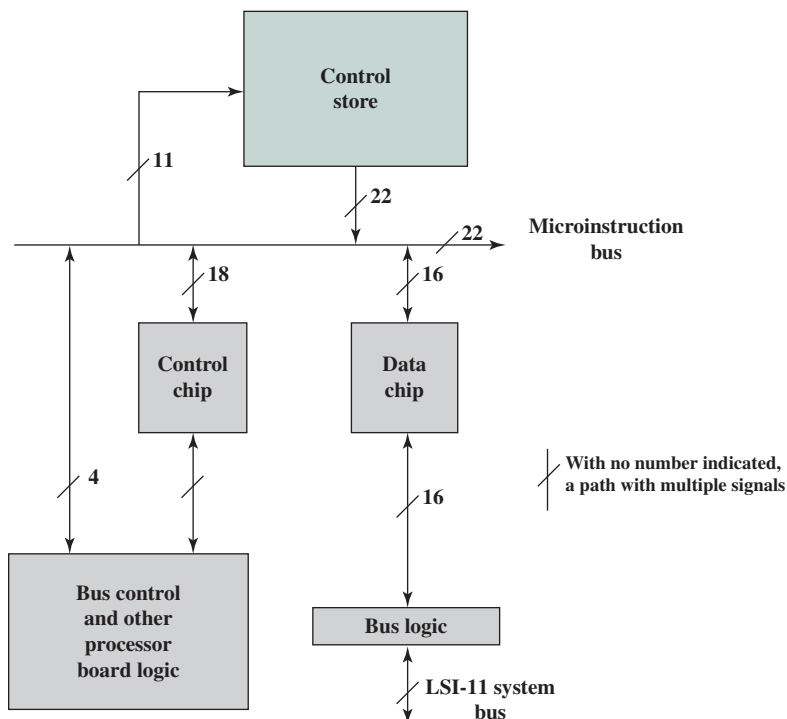


**Figure 21.13** Simplified Block Diagram of the LSI-11 Processor

codes. Sixteen of the registers are used to implement the eight 16-bit general-purpose registers of the PDP-11. Others include a program status word, memory address register (MAR), and memory buffer register. Because the ALU deals with only 8 bits at a time, two passes through the ALU are required to implement a 16-bit PDP-11 arithmetic operation. This is controlled by the microprogram.

The control store chip or chips contain the 22-bit-wide control memory. The control chip contains the logic for sequencing and executing microinstructions. It contains the control address register, the control data register, and a copy of the machine instruction register.

The MIB ties all the components together. During microinstruction fetch, the control chip generates an 11-bit address onto the MIB. Control store is accessed, producing a 22-bit microinstruction, which is placed on the MIB. The low-order 16 bits go to the data chip, while the low-order 18 bits go to the control chip. The high-order 4 bits control special processor board functions.

Figure 21.14 provides a still simplified but more detailed look at the LSI-11 control unit: the figure ignores individual chip boundaries. The address sequencing scheme described in Section 21.2 is implemented in two modules. Overall sequence control is provided by the microprogram sequence control module, which is capable

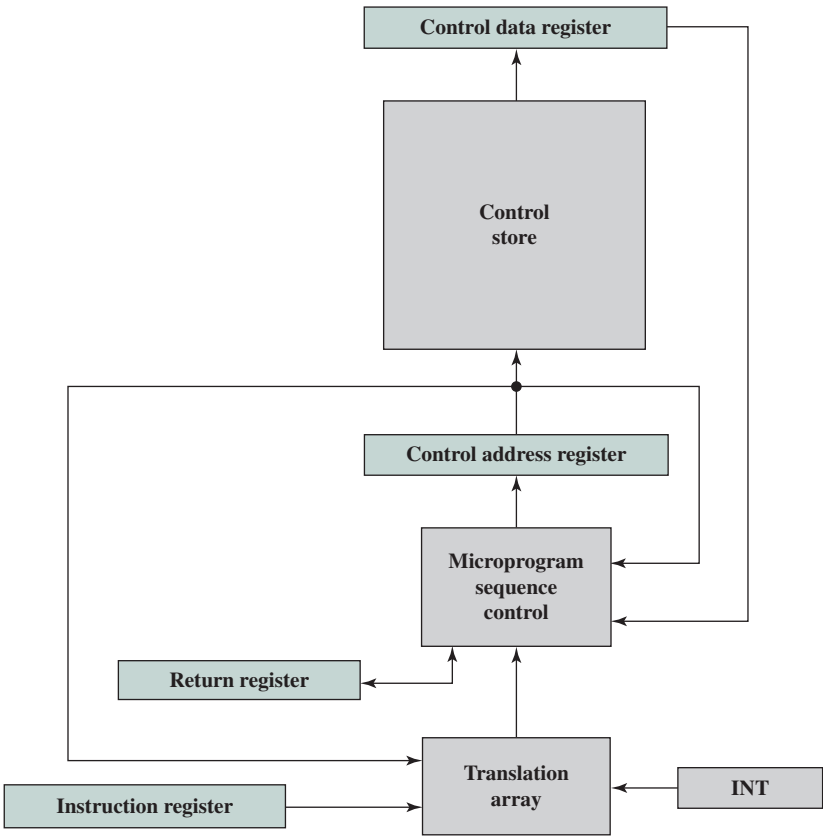

**Figure 21.14** Organization of the LSI-11 Control Unit

of incrementing the microinstruction address register and performing unconditional branches. The other forms of address calculation are carried out by a separate translation array. This is a combinatorial circuit that generates an address based on the microinstruction, the machine instruction, the microinstruction program counter, and an interrupt register.

The translation array comes into play on the following occasions:

- The opcode is used to determine the start of a microroutine.
- At appropriate times, address mode bits of the microinstruction are tested to perform appropriate addressing.
- Interrupt conditions are periodically tested.
- Conditional branch microinstructions are evaluated.

**LSI-11 MICROINSTRUCTION FORMAT** The LSI-11 uses an extremely vertical microinstruction format, which is only 22 bits wide. The microinstruction set strongly resembles the PDP-11 machine instruction set that it implements. This design was intended to optimize the performance of the control unit within the constraint of a vertical, easily programmed design. Table 21.5 lists some of the LSI-11 microinstructions.

Figure 21.15 shows the 22-bit LSI-11 microinstruction format. The high-order 4 bits control special functions on the processor board. The translate bit enables the translation array to check for pending interrupts. The load return register bit is used at the end of a microroutine to cause the next microinstruction address to be loaded from the return register.

The remaining 16 bits are used for highly encoded micro-operations. The format is much like a machine instruction, with a variable-length opcode and one or more operands.

**Table 21.5** Some LSI-11 Microinstructions

Arithmetic Operations	General Operations
Add word (byte, literal)	MOV word (byte)
Test word (byte, literal)	Jump
Increment word (byte) by 1	Return
Increment word (byte) by 2	Conditional jump
Negate word (byte)	Set (reset) flags
Conditionally increment (decrement) byte	Load G low
Conditionally add word (byte)	Conditionally MOV word (byte)
Add word (byte) with carry	
Conditionally add digits	<b>Input/Output Operations</b>
Subtract word (byte)	Input word (byte)
Compare word (byte, literal)	Input status word (byte)
Subtract word (byte) with carry	Read
Decrement word (byte) by 1	Write
	Read (write) and increment word (byte) by 1
	Read (write) and increment word (byte) by 2
	Read (write) acknowledge
	Output word (byte, status)
Logical Operations	
AND word (byte, literal)	
Test word (byte)	
OR word (byte)	
Exclusive-OR word (byte)	
Bit clear word (byte)	
Shift word (byte) right (left) with (without) carry	
Complement word (byte)	

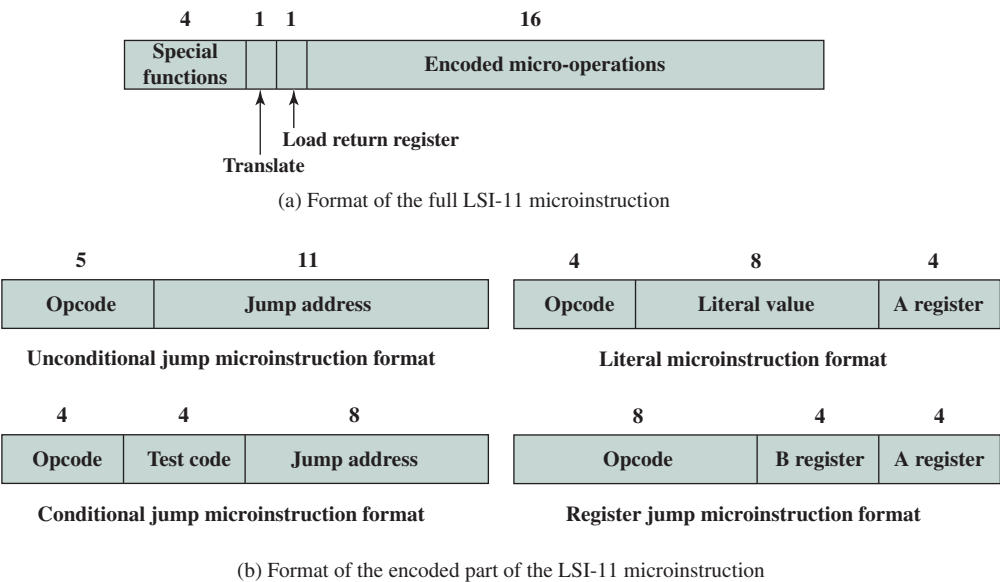


Figure 21.15 LSI-11 Microinstruction Format

IBM 3033 Microinstruction Execution

The standard IBM 3033 control memory consists of 4K words. The first half of these (0000–07FF) contain 108-bit microinstructions, while the remainder (0800–0FFF) are used to store 126-bit microinstructions. The format is depicted in Figure 21.16.

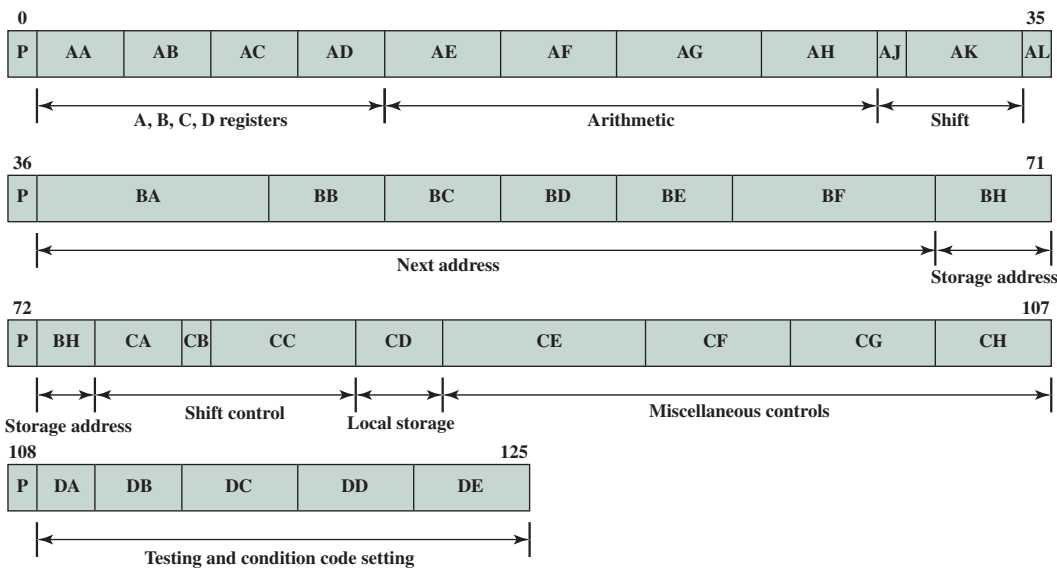


Figure 21.16 IBM 3033 Microinstruction Format



**Table 21.6** IBM 3033 Microinstruction Control Fields

<b>ALU Control Fields</b>	
AA(3)	Load A register from one of data registers
AB(3)	Load B register from one of data registers
AC(3)	Load C register from one of data registers
AD(3)	Load D register from one of data registers
AE(4)	Route specified A bits to ALU
AF(4)	Route specified B bits to ALU
AG(5)	Specifies ALU arithmetic operation on A input
AH(4)	Specifies ALU arithmetic operation on B input
AJ(1)	Specifies D or B input to ALU on B side
AK(4)	Route arithmetic output to shifter
CA(3)	Load F register
CB(1)	Activate shifter
CC(5)	Specifies logical and carry functions
CE(7)	Specifies shift amount
<b>Sequencing and Branching Fields</b>	
AL(1)	End operation and perform branch
BA(8)	Set high-order bits (00–07) of control address register
BB(4)	Specifies condition for setting bit 8 of control address register
BC(4)	Specifies condition for setting bit 9 of control address register
BD(4)	Specifies condition for setting bit 10 of control address register
BE(4)	Specifies condition for setting bit 11 of control address register
BF(7)	Specifies condition for setting bit 12 of control address register

Although this is a rather horizontal format, encoding is still extensively used. The key fields of that format are summarized in Table 21.6.

The ALU operates on inputs from four dedicated, non-user-visible registers, A, B, C, and D. The microinstruction format contains fields for loading these registers from user-visible registers, performing an ALU function, and specifying a user-visible register for storing the result. There are also fields for loading and storing data between registers and memory.

The sequencing mechanism for the IBM 3033 was discussed in Section 21.2.

## 21.4 TI 8800

The Texas Instruments 8800 Software Development Board (SDB) is a microprogrammable 32-bit computer card. The system has a writable control store, implemented in RAM rather than ROM. Such a system does not achieve the speed or

density of a microprogrammed system with a ROM control store. However, it is useful for developing prototypes and for educational purposes.

The 8800 SDB consists of the following components (Figure 21.17):

- Microcode memory
- Microsequencer
- 32-bit ALU
- Floating-point and integer processor
- Local data memory

Two buses link the internal components of the system. The DA bus provides data from the microinstruction data field to the ALU, the floating-point processor, or the microsequencer. In the latter case, the data consists of an address to be used for a branch instruction. The bus can also be used for the ALU or microsequencer to

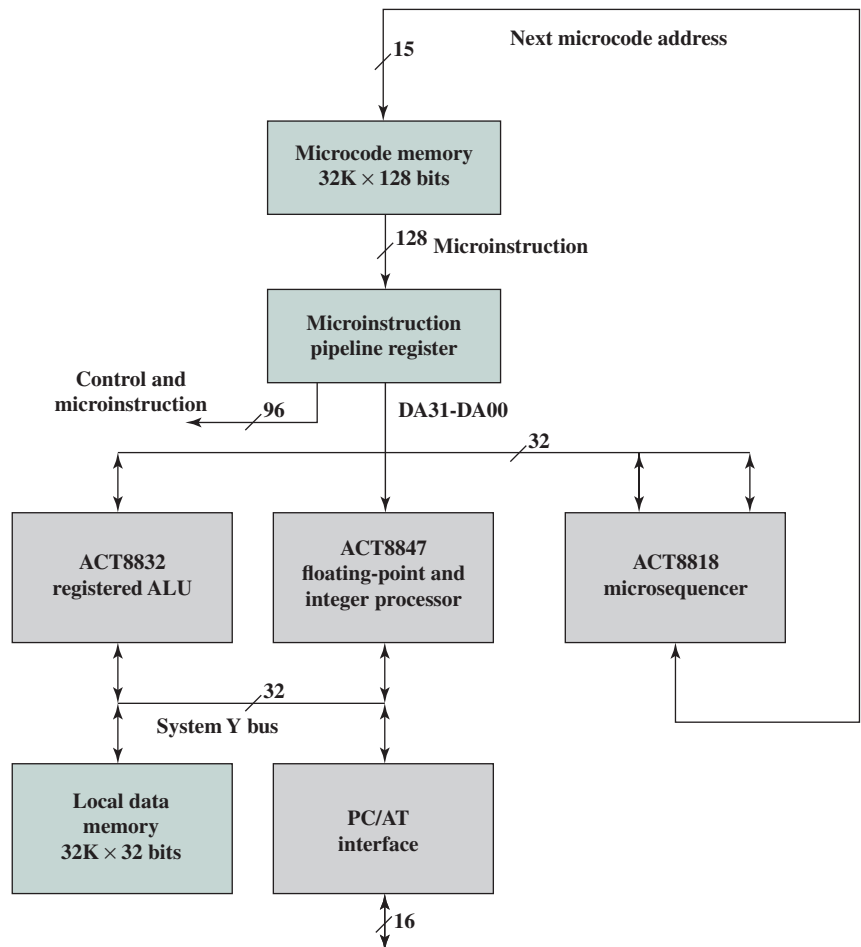


Figure 21.17 TI 8800 Block Diagram

provide data to other components. The system Y bus connects the ALU and floating-point processor to local memory and to external modules via the PC interface.

The board fits into an IBM PC-compatible host computer. The host computer provides a suitable platform for microcode assembly and debug.

## Microinstruction Format

The microinstruction format for the 8800 consists of 128 bits broken down into 30 functional fields, as indicated in Table 21.7. Each field consists of one or more bits, and the fields are grouped into five major categories:

- Control of board
- 8847 floating-point and integer processor chip
- 8832 registered ALU
- 8818 microsequencer
- WCS data field

As indicated in Figure 21.17, the 32 bits of the WCS data field are fed into the DA bus to be provided as data to the ALU, floating-point processor, or microsequencer. The other 96 bits (fields 1–27) of the microinstruction are control signals that are fed directly to the appropriate module. For simplicity, these other connections are not shown in Figure 21.17.

The first six fields deal with operations that pertain to the control of the board, rather than controlling an individual component. Control operations include the following:

- Selecting condition codes for sequencer control. The first bit of field 1 indicates whether the condition flag is to be set to 1 or 0, and the remaining 4 bits indicate which flag is to be set.
- Sending an I/O request to the PC/AT.
- Enabling local data memory read/write operations.
- Determining the unit driving the system Y bus. One of the four devices attached to the bus (Figure 21.17) is selected.

The last 32 bits are the data field, which contain information specific to a particular microinstruction.

The remaining fields of the microinstruction are best discussed in the context of the device that they control. In the remainder of this section, we discuss the microsequencer and the registered ALU. The floating-point unit introduces no new concepts and is skipped.

## Microsequencer

The principal function of the 8818 microsequencer is to generate the next microinstruction address for the microprogram. This 15-bit address is provided to the microcode memory (Figure 21.17).

The next address can be selected from one of five sources:

1. The microprogram counter (MPC) register, used for repeat (reuse same address) and continue (increment address by 1) instructions.

**Table 21.7** TI 8800 Microinstruction Format

Field Number	Number of Bits	Description
<b>Control of Board</b>		
1	5	Select condition code input
2	1	Enable/disable external I/O request signal
3	2	Enable/disable local data memory read/write operations
4	1	Load status/do no load status
5	2	Determine unit driving Y bus
6	2	Determine unit driving DA bus
<b>8847 Floating-Point and Integer Processing Chip</b>		
7	1	C register control: clock, do not clock
8	1	Select most significant or least significant bits for Y bus
9	1	C register data source: ALU, multiplexer
10	4	Select IEEE or FAST mode for ALU and MUL
11	8	Select sources for data operands: RA registers, RB registers, P register, 5 register, C register
12	1	RB register control: clock, do not clock
13	1	RA register control: clock, do not clock
14	2	Data source confirmation
15	2	Enable/disable pipeline registers
16	11	8847 ALU function
<b>8832 Registered ALU</b>		
17	2	Write enable/disable data output to selected register: most significant half, least significant half
18	2	Select register file data source: DA bus, DB bus, ALU Y MUX output, system Y bus
19	3	Shift instruction modifier
20	1	Carry in: force, do not force
21	2	Set ALU configuration mode: 32, 16, or 8 bits
22	2	Select input to 5 multiplexer: register file, DB bus, MQ register
23	1	Select input to R multiplexer: register file, DA bus
24	6	Select register in file C for write
25	6	Select register in file B for read
26	6	Select register in file A for write
27	8	ALU function
<b>8818 Microsequencer</b>		
28	12	Control input signals to the 8818
<b>WCS Data Field</b>		
29	16	Most significant bits of writable control store data field
30	16	Least significant bits of writable control store data field

2. The stack, which supports microprogram subroutine calls as well as iterative loops and returns from interrupts.
3. The DRA and DRB ports, which provide two additional paths from external hardware by which microprogram addresses can be generated. These two ports are connected to the most significant and least significant 16 bits of the DA bus, respectively. This allows the microsequencer to obtain the next instruction address from the WCS data field of the current microinstruction or from a result calculated by the ALU.
4. Register counters RCA and RCB, which can be used for additional address storage.
5. An external input onto the bidirectional Y port to support external interrupts.

Figure 21.18 is a logical block diagram of the 8818. The device consists of the following principal functional groups:


- A 16-bit microprogram counter (MPC) consisting of a register and an incrementer.
- Two register counters, RCA and RCB, for counting loops and iterations, storing branch addresses, or driving external devices.
- A 65-word by 16-bit stack, which allows microprogram subroutine calls and interrupts.
- An interrupt return register and Y output enable for interrupt processing at the microinstruction level.
- A Y output multiplexer by which the next address can be selected from MPC, RCA, RCB, external buses DRA and DRB, or the stack.

**REGISTERS/COUNTERS** The registers RCA and RCB may be loaded from the DA bus, either from the current microinstruction or from the output of the ALU. The values may be used as counters to control the flow of execution and may be automatically decremented when accessed. The values may also be used as microinstruction addresses to be supplied to the Y output multiplexer. Independent control of both registers during a single microinstruction cycle is supported with the exception of simultaneous decrement of both registers.

**STACK** The stack allows multiple levels of nested calls or interrupts, and it can be used to support branching and looping. Keep in mind that these operations refer to the control unit, not the overall processor, and that the addresses involved are those of microinstructions in the control memory.

Six stack operations are possible:

1. Clear, which sets the stack pointer to zero, emptying the stack;
2. Pop, which decrements the stack pointer;
3. Push, which puts the contents of the MPC, interrupt return register, or DRA bus onto the stack and increments the stack pointer;
4. Read, which makes the address indicated by the read pointer available at the Y output multiplexer;

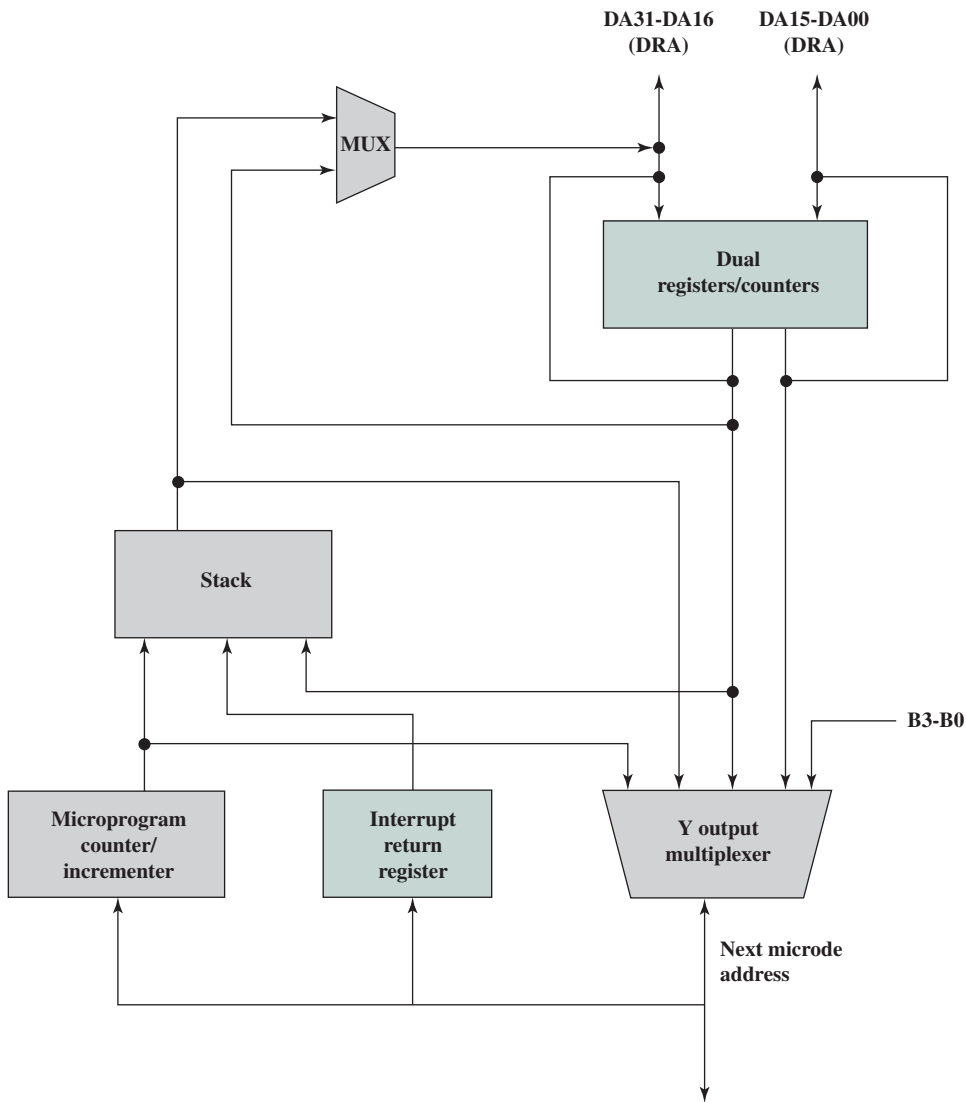

**Figure 21.18** TI 8818 Microsequencer

5. Hold, which causes the address of the stack pointer to remain unchanged;
6. Load stack pointer, which inputs the seven least significant bits of DRA to the stack pointer.

**CONTROL OF MICROSEQUENCER** The microsequencer is controlled primarily by the 12-bit field of the current microinstruction, field 28 (Table 21.7). This field consists of the following subfields:

- **OSEL (1 bit):** Output select. Determines which value will be placed on the output of the multiplexer that feeds into the DRA bus (upper-left-hand corner of

Figure 21.18). The output is selected to come from either the stack or from register RCA. DRA then serves as input to either the Y output multiplexer or to register RCA.

- **SELDR (1 bit):** Select DR bus. If set to 1, this bit selects the external DA bus as input to the DRA/DRB buses. If set to 0, selects the output of the DRA multiplexer to the DRA bus (controlled by OSEL) and the contents of RCB to the DRB bus.
- **ZEROIN (1 bit):** Used to indicate a conditional branch. The behavior of the microsequencer will then depend on the condition code selected in field 1 (Table 21.7).
- **RC2–RC0 (3 bits):** Register controls. These bits determine the change in the contents of registers RCA and RCB. Each register can either remain the same, decrement, or load from the DRA/DRB buses.
- **S2–S0 (3 bits):** Stack controls. These bits determine which stack operation is to be performed.
- **MUX2–MUX0:** Output controls. These bits, together with the condition code if used, control the Y output multiplexer and therefore the next microinstruction address. The multiplexer can select its output from the stack, DRA, DRB, or MPC.

These bits can be set individually by the programmer. However, this is typically not done. Rather, the programmer uses mnemonics that equate to the bit patterns that would normally be required. Table 21.8 lists the 15 mnemonics for field 28. A microcode assembler converts these into the appropriate bit patterns.

**Table 21.8** TI 8818 Microsequencer Microinstruction Bits (Field 28)

Mnemonic	Value	Description
RST8818	00000000110	Reset Instruction
BRA88181	011000111000	Branch to DRA Instruction
BRA88180	010000111110	Branch to DRA Instruction
INC88181	000000111110	Continue Instruction
INC88180	001000001000	Continue Instruction
CAL88181	010000110000	Jump to Subroutine at Address Specified by DRA
CAL88180	010000101110	Jump to Subroutine at Address Specified by DRA
RET8818	000000011010	Return from Subroutine
PUSH8818	000000110111	Push Interrupt Return Address onto Stack
POP8818	100000010000	Return from Interrupt
LOADDRA	000010111110	Load DRA Counter from DA Bus
LOADDRB	000110111110	Load DRB Counter from DA Bus
LOADDRAB	000110111100	Load DRA/DRB
DECRDRA	010001111100	Decrement DRA Counter and Branch If Not Zero
DECRDRB	010101111100	Decrement DRB Counter and Branch If Not Zero

As an example, the instruction INC88181 is used to cause the next microinstruction in sequence to be selected, if the currently selected condition code is 1. From Table 21.8, we have

$$\text{INC88181} = 000000111110$$

which decodes directly into

- **OSEL = 0:** Selects RCA as output from DRA output MUX; in this case the selection is irrelevant.
- **SELDR = 0:** As defined previously; again, this is irrelevant for this instruction.
- **ZEROIN = 0:** Combined with the value for MUX, indicates no branch should be taken.
- **R = 000:** Retain current value of RA and RC.
- **S = 111:** Retain current state of stack.
- **MUX = 110:** Choose MPC when condition code = 1, DRA when condition code = 0.

### Registered ALU

The 8832 is a 32-bit ALU with 64 registers that can be configured to operate as four 8-bit ALUs, two 16-bit ALUs, or a single 32-bit ALU.

The 8832 is controlled by the 39 bits that make up fields 17 through 27 of the microinstruction (Table 21.7); these are supplied to the ALU as control signals. In addition, as indicated in Figure 21.17, the 8832 has external connections to the 32-bit DA bus and the 32-bit system Y bus. Inputs from the DA can be provided simultaneously as input data to the 64-word register file and to the ALU logic module. Input from the system Y bus is provided to the ALU logic module. Results of the ALU and shift operations are output to the DA bus or the system Y bus. Results can also be fed back to the internal register file.

Three 6-bit address ports allow a two-operand fetch and an operand write to be performed within the register file simultaneously. An MQ shifter and MQ register can also be configured to function independently to implement double-precision 8-bit, 16-bit, and 32-bit shift operations.

Fields 17 through 26 of each microinstruction control the way in which data flows within the 8832 and between the 8832 and the external environment. The fields are as follows:

- 17. Write Enable.** These two bits specify write 32 bits, 16 most significant bits, 16 least significant bits, or do not write into register file. The destination register is defined by field 24.
- 18. Select Register File Data Source.** If a write is to occur to the register file, these two bits specify the source: DA bus, DB bus, ALU output, or system Y bus.
- 19. Shift Instruction Modifier.** Specifies options concerning supplying end fill bits and reading bits that are shifted during shift instructions.
- 20. Carry In.** This bit indicates whether a bit is carried into the ALU for this operation.



- 21. ALU Configuration Mode.** The 8832 can be configured to operate as a single 32-bit ALU, two 16-bit ALUs, or four 8-bit ALUs.
- 22. S Input.** The ALU logic module inputs are provided by two internal multiplexers referred to as the S and R multiplexers. This field selects the input to be provided by the S multiplexer: register file, DB bus, or MQ register. The source register is defined by field 25.
- 23. R Input.** Selects input to be provided by the R multiplexer: register file or DA bus.
- 24. Destination Register.** Address of register in register file to be used for the destination operand.
- 25. Source Register.** Address of register in register file to be used for the source operand, provided by the S multiplexer.
- 26. Source Register.** Address of register in register file to be used for the source operand, provided by the R multiplexer.

Finally, field 27 is an 8-bit opcode that specifies the arithmetic or logical function to be performed by the ALU. Table 21.9 lists the different operations that can be performed.

As an example of the coding used to specify fields 17 through 27, consider the instruction to add the contents of register 1 to register 2 and place the result in register 3. The symbolic instruction is

CONT11 [17], WELH, SELRYFYMX, [24], R3, R2, R1, PASS + ADD  
 The assembler will translate this into the appropriate bit pattern. The individual components of the instruction can be described as follows:

- CONT11 is the basic NOP instruction.
- Field [17] is changed to WELH (write enable, low and high), so that a 32-bit register is written into.
- Field [18] is changed to SELRFYMX to select the feedback from the ALU Y MUX output.
- Field [24] is changed to designate register R3 for the destination register.
- Field [25] is changed to designate register R2 for one of the source registers.
- Field [26] is changed to designate register R1 for one of the source registers.
- Field [27] is changed to specify an ALU operation of ADD. The ALU shifter instruction is PASS; therefore, the ALU output is not shifted by the shifter.

Several points can be made about the symbolic notation. It is not necessary to specify the field number for consecutive fields. That is,

CONT11 [17], WELH, [18], SELRFYMX

can be written as

CONT11 [17], WELH, SELRFYMX

because SELRFYMX is in field 18.

ALU instructions from Group 1 of Table 21.9 must always be used in conjunction with Group 2. ALU instructions from Groups 3 to 5 must not be used with Group 2.

**Table 21.9** TI 8832 Registered ALU Instruction Field (Field 27)

Group 1		Function
ADD	H#01	$R + S + C_n$
SUBR	H#02	$(NOT\ R) + S + C_n$
SUBS	H#03	$R = (NOT\ S) + C_n$
INSC	H#04	$S + C_n$
INCNS	H#05	$(NOT\ S) + C_n$
INCR	H#06	$R + C_n$
INCNR	H#07	$(NOT\ R) + C_n$
XOR	H#09	$R\ XOR\ S$
AND	H#0A	$R\ AND\ S$
OR	H#0B	$R\ OR\ S$
NAND	H#0C	$R\ NAND\ S$
NOR	H#0D	$R\ NOR\ S$
ANDNR	H#0E	$(NOT\ R)\ AND\ S$
Group 2		Function
SRA	H#00	Arithmetic right single precision shift
SRAD	H#10	Arithmetic right double precision shift
SRL	H#20	Logical right single precision shift
SRLD	H#30	Logical right double precision shift
SLA	H#40	Arithmetic left single precision shift
SLAD	H#50	Arithmetic left double precision shift
SLC	H#60	Circular left single precision shift
SLCD	H#70	Circular left double precision shift
SRC	H#80	Circular right single precision shift
SRCD	H#90	Circular right double precision shift
MQSRA	H#A0	Arithmetic right shift MQ register
MQSRL	H#B0	Logical right shift MQ register
MQSLL	H#C0	Logical left shift MQ register
MQSLC	H#D0	Circular left shift MQ register
LOADMQ	H#E0	Load MQ register
PASS	H#F0	Pass ALU to Y (no shift operation)
Group 3		Function
SET1	H#08	Set bit 1
Set0	H#18	Set bit 0
TB1	H#28	Test bit 1
TB0	H#38	Test bit 0
ABS	H#48	Absolute value
SMTC	H#58	Sign magnitude/twos-complement

Group 3		Function
ADDI	H#68	Add immediate
SUBI	H#78	Subtract immediate
BADD	H#88	Byte add R to S
BSUBS	H#98	Byte subtract S from R
BSUBR	H#A8	Byte subtract R from S
BINCS	H#B8	Byte increment S
BINCNS	H#C8	Byte increment negative S
BXOR	H#D8	Byte XOR R and S
BAND	H#E8	Byte AND R and S
BOR	H#F8	Byte OR R and S
Group 4		Function
CRC	H#00	Cyclic redundancy character accum.
SEL	H#10	Select S or R
SNORM	H#20	Single length normalize
DNORM	H#30	Double length normalize
DIVRF	H#40	Divide remainder fix
SDIVQF	H#50	Signed divide quotient fix
SMULI	H#60	Signed multiply iterate
SMULT	H#70	Signed multiply terminate
SDIVIN	H#80	Signed divide initialize
SDIVIS	H#90	Signed divide start
SDIVI	H#A0	Signed divide iterate
UDIVIS	H#B0	Unsigned divide start
UDIVI	H#C0	Unsigned divide iterate
UMULI	H#D0	Unsigned multiply iterate
SDIVIT	H#E0	Signed divide terminate
UDIVIT	H#F0	Unsigned divide terminate
Group 5		Function
LOADFF	H#0F	Load divide/BCD flip-flops
CLR	H#1F	Clear
DUMPFF	H#5F	Output divide/BCD flip-flops
BCDBIN	H#7F	BCD to binary
EX3BC	H#8F	Excess (3 byte correction
EX3C	H#9F	Excess (3 word correction
SDIVO	H#AF	Signed divide overflow test
BINEX3	H#DF	Binary to excess – 3
NOP32	H#FF	No operation

21.5 KEY TERMS, REVIEW QUESTIONS, AND PROBLEMS

Key Terms

control memory control word firmware hard microprogramming horizontal microinstruction	microinstruction encoding microinstruction execution microinstruction sequencing microinstructions microprogram	microprogrammed control unit microprogramming language soft microprogramming unpacked microinstruction vertical microinstruction
--	---	--

Review Questions

- 21.1 What is the difference between a hardwired implementation and a microprogrammed implementation of a control unit?
- 21.2 How is a horizontal microinstruction interpreted?
- 21.3 What is the purpose of a control memory?
- 21.4 What is a typical sequence in the execution of a horizontal microinstruction?
- 21.5 What is the difference between horizontal and vertical microinstructions?
- 21.6 What are the basic tasks performed by a microprogrammed control unit?
- 21.7 What is the difference between packed and unpacked microinstructions?
- 21.8 What is the difference between hard and soft microprogramming?
- 21.9 What is the difference between functional and resource encoding?
- 21.10 List some common applications of microprogramming.

Problems

- 21.1 Describe the implementation of the multiply instruction in the hypothetical machine designed by Wilkes. Use narrative and a flowchart.
- 21.2 Assume a microinstruction set that includes a microinstruction with the following symbolic form:

$$\text{IF } (AC_0 = 1) \text{ THEN } CAR \leftarrow (C_{0-6}) \text{ ELSE } CAR \leftarrow (CAR) + 1$$

where  $AC_0$  is the sign bit of the accumulator and  $C_{0-6}$  are the first seven bits of the microinstruction. Using this microinstruction, write a microprogram that implements a Branch Register Minus (BRM) machine instruction, which branches if the AC is negative. Assume that bits  $C_1$  through  $C_n$  of the microinstruction specify a parallel set of micro-operations. Express the program symbolically.

- 21.3 A simple processor has four major phases to its instruction cycle: fetch, indirect, execute, and interrupt. Two 1-bit flags designate the current phase in a hardwired implementation.
  - a. Why are these flags needed?
  - b. Why are they not needed in a microprogrammed control unit?
- 21.4 Consider the control unit of Figure 21.7. Assume that the control memory is 24 bits wide. The control portion of the microinstruction format is divided into two fields. A micro-operation field of 13 bits specifies the micro-operations to be performed. An address selection field specifies a condition, based on the flags, that will cause a microinstruction branch. There are eight flags.

- a. How many bits are in the address selection field?
  - b. How many bits are in the address field?
  - c. What is the size of the control memory?
- 21.5** How can unconditional branching be done under the circumstances of the previous problem? How can branching be avoided; that is, describe a microinstruction that does not specify any branch, conditional or unconditional.
- 21.6** We wish to provide 8 control words for each machine instruction routine. Machine instruction opcodes have 5 bits, and control memory has 1024 words. Suggest a mapping from the instruction register to the control address register.
- 21.7** An encoded microinstruction format is to be used. Show how a 9-bit micro-operation field can be divided into subfields to specify 46 different actions.
- 21.8** A processor has 16 registers, an ALU with 16 logic and 16 arithmetic functions, and a shifter with 8 operations, all connected by an internal processor bus. Design a microinstruction format to specify the various micro-operations for the processor.